

---

## EE273 Lecture 18

### On-Chip Power Distribution

November 25, 1998

William J. Dally  
Computer Systems Laboratory  
Stanford University  
billd@csl.stanford.edu

---

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

1

## Today's Assignment

---

- Term Project
  - final project due on Wednesday 12/2
  - presentations next week on Monday 11/30 and Wednesday 12/2
- Final Exam
  - will be in Terman Auditorium
  - 8:30AM to 10:30AM
  - Thursday December 10

---

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

2

## A Quick Overview

- Power is distributed on-chip from power pads to point of use
  - from edges for peripheral-bonded chips
- Load profile is determined by characteristics of logic
  - fan-out and select
- The distribution network is sized to handle the worst-case current while keeping the IR drops within margins
- On-chip bypass capacitors can reduce the amount of metal needed for distribution
  - change *peak* requirement to *average* requirement
- Symbiotic bypass capacitors are always present
  - this is why most circuits work!
- Isolate delicate circuits from noisy circuits

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

3

## The On-Chip Power Distribution Problem

- Supply current is brought on chip at specific locations
  - on the edge for most chips which are *peripherally bonded*
  - distributed over the area of the chip for *area bonded* (C4, solder ball) chips
- Loads consume this current at different locations on the chip at different times
- There is often a large parasitic inductance associated with each bond-wire or solder-ball (0.1-10nH)
- Current is distributed from the bond pads to the loads on thin metal wires
  - $0.04\Omega/\mu$  typical
- Load currents may be very high
  - average current may be as large as 20A for very hot chips (50W at 2.5V)
  - peak current may be 4-5x this amount (100A!)
- $L di/dt$  of bond wire and IR drop across on-chip wires are often a major source of supply noise

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

4

## Power Distribution Trends

- The on-chip power distribution problem is getting *much* harder as technology evolves
- Combination of
  - lower voltages
  - higher current density
  - thinner metal layers
  - larger chips
- We are quickly approaching the point where peripheral bonding will not be adequate for high-performance chips

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

5

## Logic Current Profile

- Why does on-chip logic produce a 'spikey' current profile?
- Consider the logic that generates the current
- Current is drawn to charge gate and wire capacitance  
 $Q=CV$ ,  $E=CV^2$
- Typical behavior includes
  - circuit idle before clock edge
    - very little current
  - exponential clock amplification just before clock edge
    - exponential ramp up in current
  - flip-flops are clocked
    - current depends on activity factor
  - Fanout in a logic circuit
    - exponential ramp up in current
  - Fan-in or selection in a logic circuit
    - drop in current

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

6

## Logic Current Profile Examples (cont.)

- a memory or register array
  - fanout in decoder
  - selection of word-line
  - amplification in S/A
  - selection in multiplexer
- A carry-lookahead adder
  - modest fan-out in PGK blocks
  - fan-out in carry tree
  - fan-in in carry tree, but with amplification
  - amplification to drive output
- Control logic
  - much like the decoder
  - fan-out in the first few stages
  - then tree fanning in to flip-flops
  - often a long, serial tail
- Overall current profile is the superposition of all of these profiles

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

7

## Worst-Case vs. Average Logic Current Profile

- Current drawn is often very data dependent
  - e.g., a data path may switch 64-bits from all 0s to all 1s
  - on average only 1/4 of the bits will have this transition when there is a transition at all
- For noise analysis we must consider *worst-case* power
  - cannot allow possible, but unlikely events to cause system failure
- For battery life we may consider *average* power

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

8

## IR-Drops


- Power distribution network is designed to keep IR drop on  $V_{DD}$  and GND networks within limits
  - e.g., for 10% supply variation, can drop at most 5% on each supply
- Networks are usually designed specifically for the loads of a given chip.
- However, we can gain insight into the process by considering a uniform load
- For example, suppose current densities are
  - $J_{peak} = 0.3A/mm^2$
  - $J_{avg} = 0.05A/mm^2$
- For a peripheral bonded chip,  $V_{DD}$  and GND are usually distributed by *combs* with interdigitated fingers
  - a hierarchy of such combs is often used
- How much of a metal layer (or how many layers) do we need to distribute this power

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

9

## IR Drops, The Picture

 

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

10

## IR Drops, the Calculation

- Consider a thin *slice* of the chip, say 1mm high
- Suppose a fraction,  $k_p$ , of a metal layer is devoted to each supply
- In a slice of length  $L$ , say 16mm, current is drawn from both sides over a 8mm path
- The resistance of a 1mm length of the supply net is

$$R = \frac{R_{sq}}{k_p} = \frac{0.04}{k_p} \Omega$$

- Voltage integrates along the strip, so

$$V(x) = \frac{x^2 r_w I_{max}}{k_p L} = \frac{0.04 x^2 J_{peak}}{2 k_p}$$

This current ramps linearly, so current at point  $x$  is

$$I_{max} = \frac{L J_{peak}}{2}$$

$$I(x) = 2x I_{max} / L$$

$$V\left(\frac{L}{2}\right) = \frac{r_w L^2 J_{peak}}{8 k_p} = \frac{0.005 L^2 J_{peak}}{k_p}$$

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

11

## IR Calculation, Cont.

- So, to get  $k_p$ , for a given voltage drop,  $V$ , say 125mV we have
- Clearly this is not acceptable.

$$\begin{aligned} k_p &= \frac{r_w L^2 J_{peak}}{8V} \\ &= \frac{(0.04)(15)^2 (0.3)}{8(.125)} \\ &= 2.7 \end{aligned}$$

- This is almost 3 metal layers for each of power and GND!

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

12

## Metal Migration

- Over long distances, current density must be kept low to avoid large IR drops
- Over short distances, current density must *still* be kept low to avoid *metal migration*
- Over time, wires that carry high current densities will fail as the metal is eroded away
  - think of your wire as a fuse
- Migration threshold varies depending on process, temperature, and lifetime
- A typical number is
  - $J_{MM} = 1\text{mA}/\mu\text{m}^2$
- This is often a factor on short power buses that connect from the main bus to a point of high current use
- It can also be a factor on the output of high-current drivers
- Migration applies to vias as well as wires

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

13

## On-Chip Bypass Capacitors


- The good news is that the power distribution network doesn't really need to carry all of the peak current
- Much of the difference between peak and average current may be supplied by local, on-chip bypass capacitors
- Bypass capacitors are also critical in mitigating the effects of the supply bond-wire inductance
- Suppose we want to distribute power on just two metal layers ( $k_p=1$ ) but keep the drop on each supply to 0.125V
  - Need to reduce peak current from  $0.3\text{A}/\text{mm}^2$  to  $0.1\text{A}/\text{mm}^2$

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

14
 
## On-Chip Bypass Capacitors Current Profile



$$Q = \left(\frac{2}{3}\right)^2 (0.3 \text{ A/mm}^2) (1 \times 10^{-9}) (0.5) = 67 \text{ pC/mm}^2$$

$$C = \frac{Q}{\Delta V} = \frac{67 \text{ pC/mm}^2}{0.25 \text{ V}} = 267 \text{ pF/mm}^2$$

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

15

## On Chip Bypass Capacitors

- We need a bypass capacitor of about 0.25nF for each 1mm<sup>2</sup> area of the chip
- For comparison, an MOS capacitor covering a 1mm<sup>2</sup> area has a capacitance of about 5nF/mm<sup>2</sup>
- So, our bypass capacitor uses 5% of the silicon area!
- Can be made much smaller with local regulation

EE273, L18, Nov 25, 1998


Copyright (C) by William J. Dally, All Rights Reserved

16


 
## Symbiotic Bypass Capacitors

- Where are the bypass capacitors in this picture?
- Gates that are not switching at a given instant in time act as *symbiotic* bypass capacitors
- If only one gate in 60 switches at a given instant, the bypass capacitance is 30 times the switched capacitance



EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

17

## Power Supply Isolation

- Chips often contain
  - **noisy circuits**
    - pad-drivers
    - clock generators
    - large RAM arrays
  - **noise-sensitive circuits**
    - PLLs and DLLs
    - receive amplifiers
    - etc...
- We would like to isolate the noise sensitive circuits from the noise generated by the noisy circuits
- To do this we need to make sure the two circuits share as little of the power distribution network as possible
- Typically provide separate power and/or GND pins
  - **quiet GND and  $V_{DD}$**

EE273, L18, Nov 25, 1998

Copyright (C) by William J. Dally, All Rights Reserved

18

## Next Time

---

- Project Presentations