
EE273 Lecture 3 More about Wires Lossy Wires, Multi-Drop Buses, and Balanced Lines

September 30, 1998

William J. Dally
Computer Systems Laboratory
Stanford University
billd@csl.stanford.edu

EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

1

Today's Assignment

- Reading
 - Sections 3.6 and 3.7
 - Complete before class on Monday
- Problem Set 2
 - do exercises 3-2, 3-6, 3-7, and 3-16
 - run SPICE to verify your answer for all four problems
 - due at start of class on Wednesday 10/7

EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

2

A Quick Overview

- Real transmission lines have loss
 - resistance of conductors
 - conductance of insulators
- RC lines are an extreme case
 - propagation governed by heat equation
 - delay and rise time are quadratic with length
- This loss distorts the waveform
 - rapid rise to AC signal level
 - long tail to DC signal level
- This distortion reduces the eye opening and hence the noise immunity
- Loss is frequency dependent
 - skin effect $R \sim f^{1/2}$
 - dielectric absorption $G \sim f$
- Multidrop buses have stubs and lumped loads
 - clean signal propagation is possible only when rise time is long compared to length of
 - stubs
 - space between loads
 - distributed capacitance reduces impedance significantly


EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

3

RC Transmission Lines

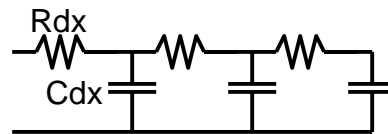- Most real lines dissipate power
 - resistance of conductors
 - conductance of insulator
- RC lines are an extreme case
 - $R \gg j\omega L$
 - typical of on-chip wires
 - $R = 150\text{k}\Omega/\text{m}$
 - $L = 600\text{nH}/\text{m}$
 - $\omega_1 = 2.5 \times 10^{11}$ (40GHz)
 - propagation is governed by the heat equation



$$\frac{\partial^2 V}{\partial x^2} = RC \frac{\partial V}{\partial t}$$


EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

4

Propagation in RC Transmission Lines

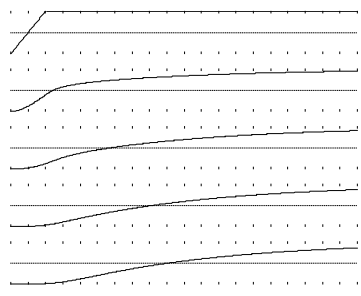- Signal is dispersed as it propagates down a line
 - R increases with length, d
 - C increases with d
 - delay and rise time increase with RC and thus with d^2
 - for a typical wire
 - R = 150K Ω /m, C=200pF/m
 - $\tau = RC = 30\mu\text{s}/\text{m}^2 = 30\text{ps}/\text{mm}^2$




$$t_d \approx 0.4d^2RC$$

$$t_r \approx d^2RC$$

EE273, L3, Sept 30, 1998 Copyright (C) by William J. Dally, All Rights Reserved 5


Lossy Transmission Lines

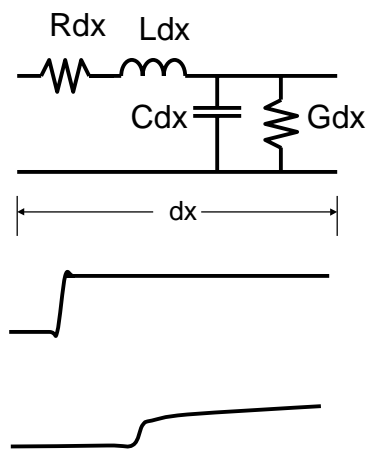- LC lines with resistance and conductance
 - propagation mostly by wave
 - some by diffusion
- R and G dissipation
 - reduces the amplitude of the signal
 - disperses the signal
 - fast rise to AC attenuation
 - slow tail to DC attenuation
- Resistance and conductance depend on frequency
 - we will ignore this for now



EE273, L3, Sept 30, 1998 Copyright (C) by William J. Dally, All Rights Reserved 6



Step Response of 1m 8mil Strippguide

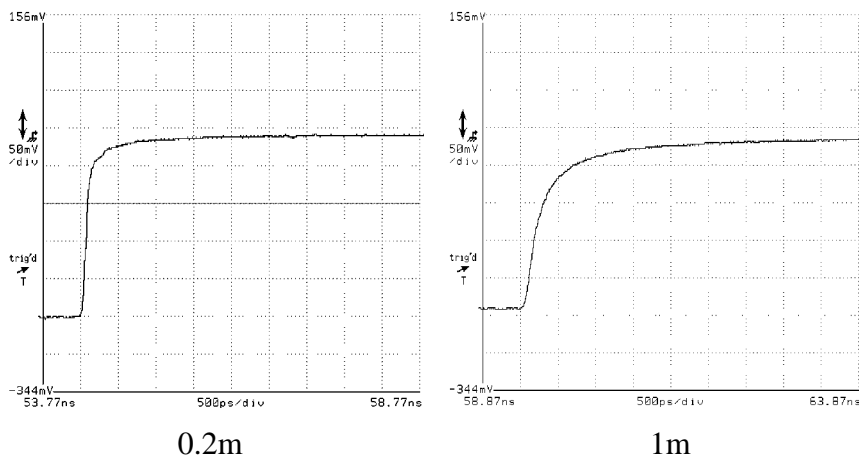

EE273, L3, Sept 30, 1998

7

Simple Model of Resistive Attenuation

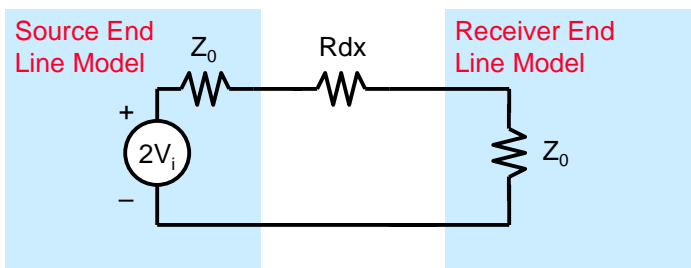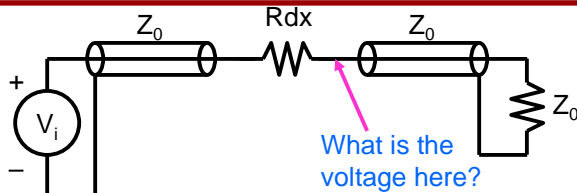


EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

8

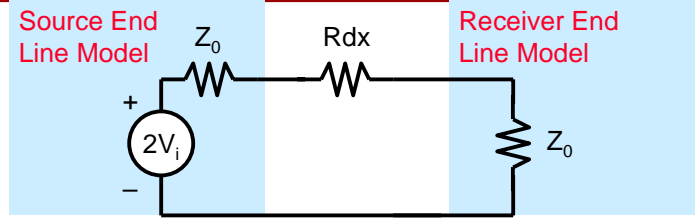Simple Model of Resistive Attenuation (2)



$$\frac{V_i(x+dx)}{V_i(x)} = \frac{Z_0}{2Z_0 + Rdx} = \frac{1}{1 + Rdx/2Z_0}$$

Attenuation Constant


$$\frac{V_i(x+ndx)}{V_i(x)} = \left(\frac{1}{1 + Rdx/2Z_0} \right)^n$$

$$\alpha = \frac{R}{2Z_0}$$

$$\frac{V_i(x)}{V_i(0)} \approx \exp\left(-x\left(\frac{R}{2Z_0}\right)\right)$$

See the text for an alternative derivation


Zero-th Order Waveform

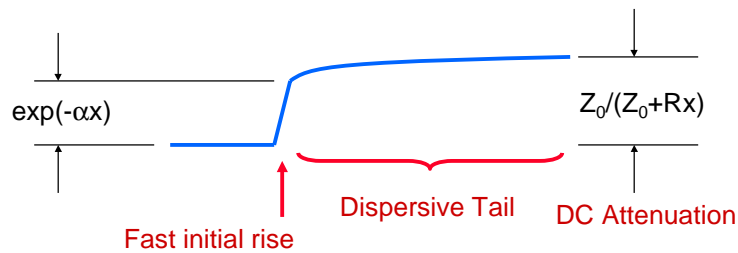

Q: So why worry about attenuation?

A: It closes the eye opening!

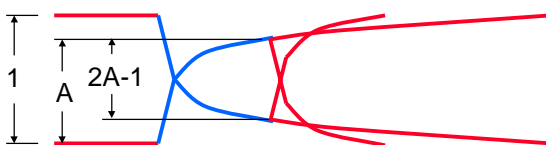- Critical parameter is what fraction of swing, A is achieved in one bit time
- Eye opening is reduced to $B = 2A - 1$
- No eye opening at 50% attenuation
- Significant degradation of margins at lower levels of attenuation



EE273, L3, Sept 30, 1998


Copyright (C) by William J. Dally, All Rights Reserved

11

Skin Effect Resistance

- Beauty is only skin deep - so is current
 - current density drops off exponentially with depth
- Skin depth decreases with frequency, $f^{-1/2}$
- Model as if all current flowed in δ -thick outer layer of conductor

$$\delta = (\pi f \mu \sigma)^{-1/2}$$

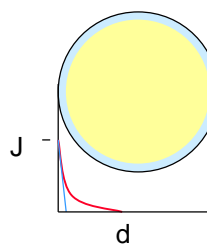

$$J = \exp\left(-\frac{d}{\delta}\right)$$

EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

12

Skin-Effect Resistance

- Effect does not occur until frequency, f_s , at which skin depth equals conductor radius
- Above f_s , R and A increase as the square-root of frequency


$$R(f) = \frac{R_{DC}}{2} \left(\frac{f}{f_s} \right)$$

EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

13

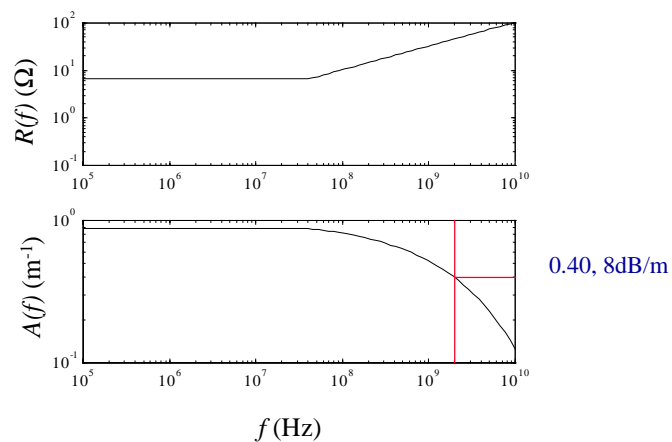Resistance and Attenuation of 5mil 0.5oz 50Ω Strippguide



EE273, L3, Sept 30, 1998

14

Dielectric Absorption

- High frequency signals *jiggle* molecules in the insulator
 - insulator *absorbs* signal energy
- This effect is approximately linear with frequency and is modeled as a conductance
- Dielectric loss is often specified in terms of a *loss tangent*, $\tan(\delta)$

$$\tan \delta = \frac{G}{\omega C}$$

$$\alpha_D = \frac{GZ_0}{2}$$

$$= \pi f \tan \delta \sqrt{LC}$$

$$= \frac{\pi \sqrt{\epsilon_r} f \tan \delta}{c}$$


material	$\tan \delta$
FR4	0.035
Polyimide	0.025
GETEK	0.010
Teflon	0.001

EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

15

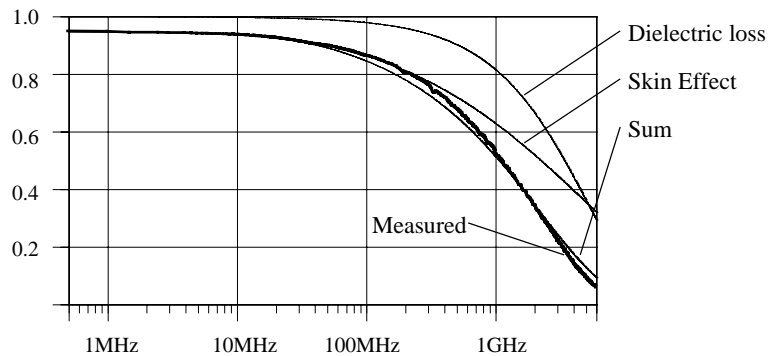Skin effect resistance and dielectric absorption



1m 8mil 50Ω stripguide with GETEK dielectric

EE273, L3, Sept 30, 1998

16

The Bd^2 Constant

- Suppose you can tolerate a certain attenuation, A
 - eye opening is $2A-1$
- At a certain bandwidth, B_1 , attenuation A is achieved with a distance of 1m
- As bandwidth is increased, resistance, and hence attenuation, increases as $B^{1/2}$
- So distance must be decreased by a proportional amount


$$A(B_1) = A_1$$

$$A(B, d) = A_1 d \left(\frac{B}{B_1} \right)^{1/2}$$

$$Bd^2 = B_1$$

Doubling distance cuts bandwidth by a factor of 4

Multi-drop Buses

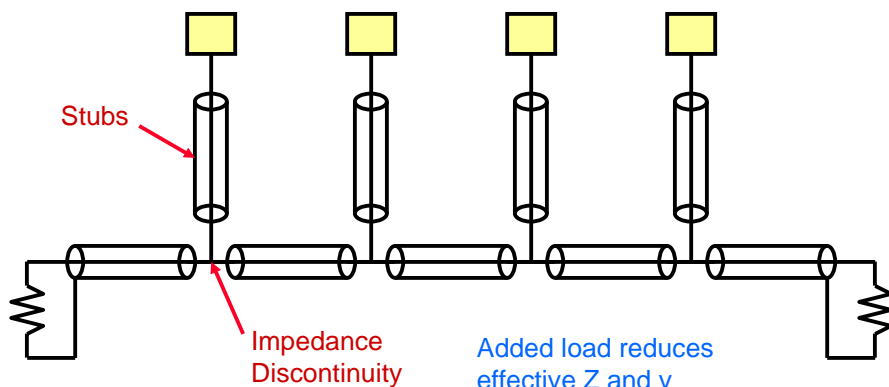

Multi-Drop Buses

- Consider a typical bus
 - 50 Ω PC board traces
 - C = 100pF/m, L=300nH/m
 - Stubs are 10cm long (0.7ns)
 - 20pF load at end
 - Spacing between modules is 3cm
- Constraints:
 - rise time must be *long* compared to stub length (>3ns) and spacing (>1ns)
 - 30pF each 3cm brings C to 1100pF/m
 - Z = 16.5 Ω , v=5.5 x 10⁷ m/s
 - driver sees 8.25 Ω
- Bus speed is limited by geometry of the bus
 - stub length
 - stub spacing
- Leaving a module 'unplugged' causes a discontinuity
- Point-to-point signaling
 - is electrically much cleaner
 - allows concurrent transfers
- 'Just say no' to buses

EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

19

Next Time

- Balanced lines
 - return current induces voltage across signal return inductance
 - if return and signal have identical L and C line is balanced
 - even and odd modes of propagation
- Modeling Wires
 - given a *real* wire, make a SPICE model
- Measurement Techniques
 - time-domain reflectometry
 - time-domain transmission measurements
 - network analysis

EE273, L3, Sept 30, 1998

Copyright (C) by William J. Dally, All Rights Reserved

20