

---

## EE273 Lecture 7

### Introduction to Signaling

October 14, 1998

William J. Dally  
Computer Systems Laboratory  
Stanford University  
billd@csl.stanford.edu

---

EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

1

## Today's Assignment

---

- Problem Set 4
  - Exercises 7-2, 7-7, and 7-8 + Series terminated driver
  - Due at start of class next Wednesday 10/21
  - See the problem set on the web for details
- Reading
  - Sections 7.4 and 7.5
  - Complete before class on Monday
- Reminder
  - demo during review session this Friday 10/16
    - Gates B03 9:00 to 9:50
  - midterm is in the evening on 10/26
  - no class on 10/26

---

EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

2

## A Quick Overview

- Introduction to Signaling
- transmission method
  - current vs. voltage
  - bipolar vs. unipolar
- termination scheme
  - parallel, source, both, unterminated
- references
  - 0 reference, transmitter reference, receiver reference
- source termination
  - use reflection to double signal amplitude
- differential signaling
  - 1.3-1.8x as many pins but many nice properties


EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

3

## An Example Signaling System

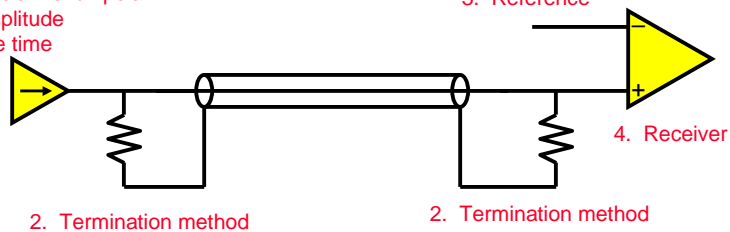
1. Transmitter:  
output impedance  
bipolar vs. unipolar  
amplitude  
rise time



EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

4

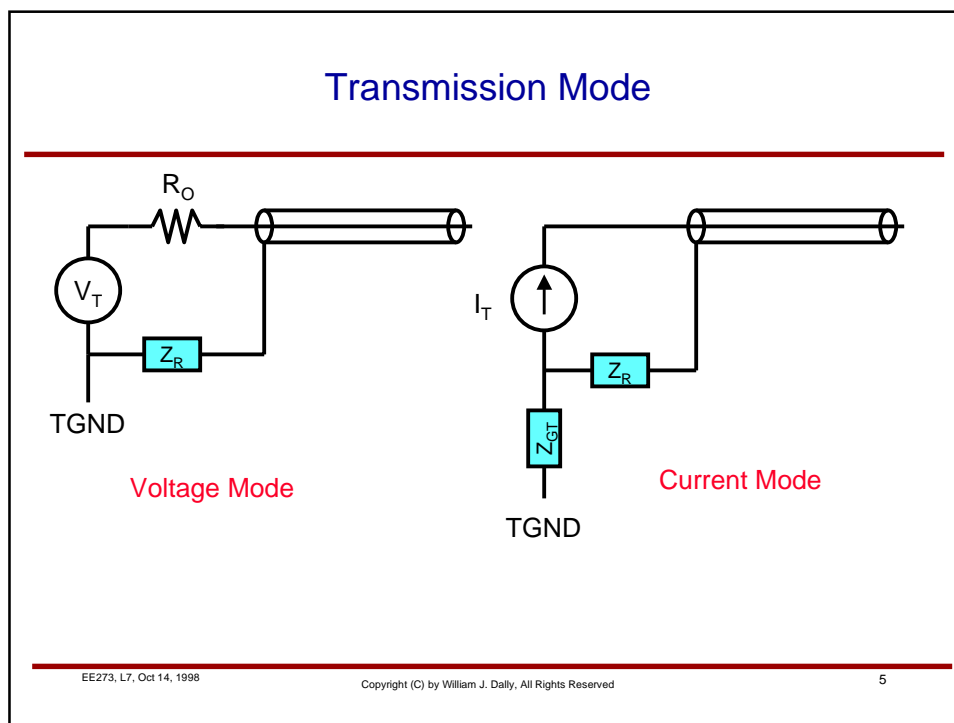

### Voltage Mode vs. Current Mode


---

- In reality a continuum as  $R_O$  varies from 0 to  $\infty$ .
- Both launch the same signal into the line  $V_i = I_i Z_0$
- Main differences are
  - ease of generation
    - much easier to generate a small current than a small voltage
    - especially with bipolar signaling
  - coupling of supply noise
  - coupling of return noise

EE273, L7, Oct 14, 1998
Copyright (C) by William J. Dally, All Rights Reserved
6
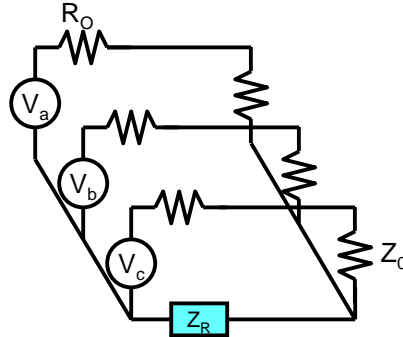
## Output Resistance and Signal Return Crosstalk

- Solve for signal return crosstalk using superposition
  - voltage source  $V_a$  active, all others shorted
  - How much current goes down other lines?
  - Other lines are in parallel with  $Z_R$ 
    - form a current divider



$$Z_X = Z_R \parallel \left( \frac{R_O + Z_0}{N-1} \right)$$


$$= \frac{Z_R (R_O + Z_0)}{(N-1)Z_R + R_O + Z_0}$$

EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

7

## Signal Return Crosstalk (continued)

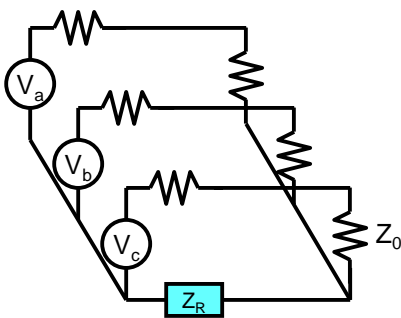

$$Z_X = Z_R \parallel \left( \frac{R_O + Z_0}{N-1} \right)$$

$$= \frac{Z_R (R_O + Z_0)}{(N-1)Z_R + R_O + Z_0}$$

$$I_X = I_a \left( \frac{Z_X}{R_O + Z_0} \right)$$

$$= I_a \left( \frac{Z_R}{(N-1)Z_R + R_O + Z_0} \right)$$


$$k_{RX} = \left( \frac{Z_R}{(N-1)Z_R + R_O + Z_0} \right)$$

EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

8

### Signal Return Crosstalk (concluded)

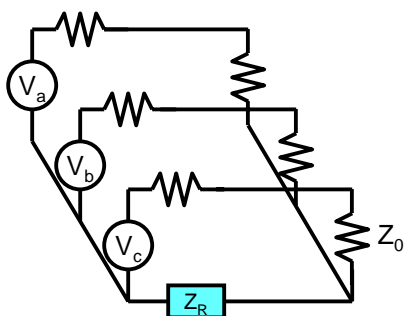

$$k_{RX} \leq \left( \frac{Z_R}{R_O + Z_0} \right)$$


- Since  $Z_R$  is usually  $\ll R_O + Z_0$  we can approximate the formula with a simple ratio
- High output impedance reduces return crosstalk
  - $Z_R/Z_0$  for voltage mode  $R=0$
  - $Z_R/2Z_0$  for matched  $R=Z$
  - $\infty$  for current mode  $R=\infty$
- Even with current mode signaling, however, it is advantageous to have a source termination:  $R_O=Z_0$

EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

9

### Source Terminated Current Mode

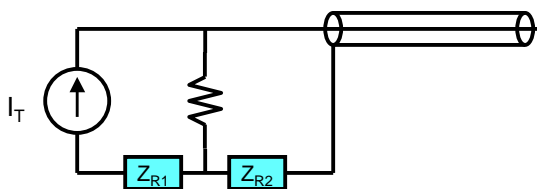

What is  $k_{RX}$  for this configuration?


EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

10
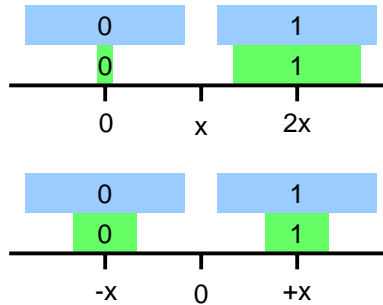
## Bipolar vs. Unipolar Signaling

- Unipolar signaling
  - logic 0 is 0 mA
  - logic 1 is 2x mA
- Bipolar signaling
  - logic 0 is -x mA
  - logic 1 is x mA
  - gives balanced transmitter offsets
    - same for 0 and 1
  - allows the use of 0 as a receiver reference
- Same applies to voltage-mode x V rather than x mA




EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

11
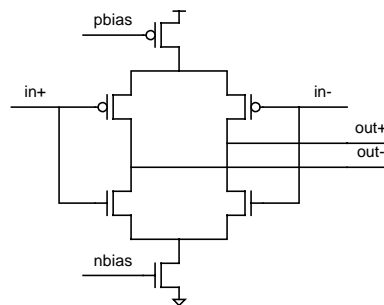
## A Typical Bipolar Current-Mode Driver

- Steers 5mA current between out+ and out-
  - constant draw from both current sources
- Relatively small devices
  - about 10 $\mu$ m/0.35 $\mu$ m
  - termination is much bigger
- Use directly for differential signaling
- Tie out- to return for single-ended signaling
- Half the supply power of a unipolar driver with the same signal swing




EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

12
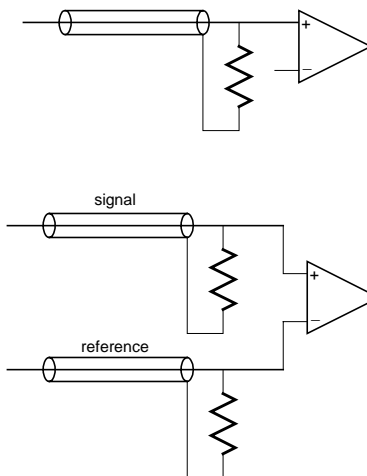
## References

- Receiver compares received voltage or current to a *reference* to discriminate between symbols
- Errors in reference add directly to independent noise
- Several ways to generate a reference
  - use 0 (bipolar signaling)
  - derive from receiver power supply
  - send from transmitter




EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

13
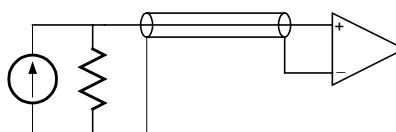
## Source Termination (Without receiver termination)

- What is response at S and R to 10mA current step on source?
  - assume line and termination are both  $50\Omega$
- What about a narrow current pulse?




EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

14
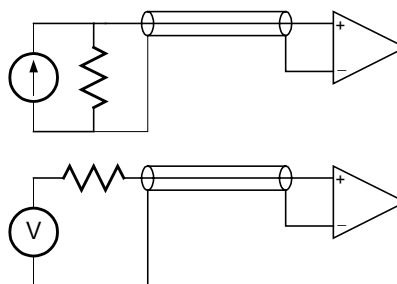
## Source Termination Advantages and Disadvantages

- Power
  - current driver
    - half the power as terminating at both ends
  - voltage driver
    - half the power as parallel termination
    - no static power
- Cross talk
  - rejects near-end cross talk
  - no difference in response to far-end cross talk
- Proper waveform is observed only at receiver



- More sensitive to inter-symbol interference
  - one bounce vs. two



EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

15
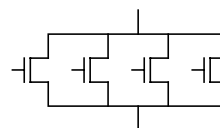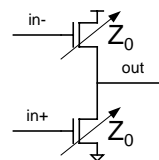
## A Voltage-Mode Source Terminated Driver

- Looks like an simple driver, but...
  - Must digitally trim FETs to get  $R_T = Z_0$  to an acceptable tolerance
  - Need a very low transmitter supply (250mV) to get an appropriate signal level
    - $\pm 125\text{mV}$  would be better
    - if transmit supply is generated with a switching regulator, very low power is possible



EE273, L7, Oct 14, 1998


Copyright (C) by William J. Dally, All Rights Reserved

16


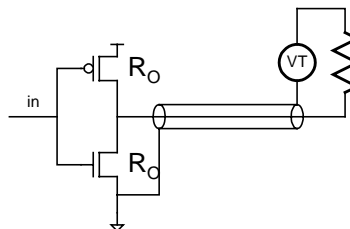
## Underterminated Sources

- Conventional inverter drivers
  - have too high an output resistance ( $400\Omega$  typical)
  - operate off of too high a supply voltage (3.3V typical)
- If the inverter tries to drive a line to full swing, it must *ring-up* the line resulting in large delay
- These inverters can be used as *underterminated* sources (high output impedance) to directly drive a  $50\Omega$  line with a low swing



- Line is parallel terminated to mid-rail supply,  $V_T$ .
- What are the signal levels on the line?
- Why mid-rail terminate?


EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

17
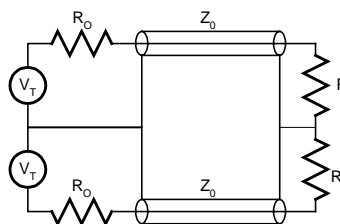
## Differential Signaling

- A *differential* signal is sent as a difference in voltage or current between two lines
- Typically a positive signal is sent on one line and its complement on the other line
- This uses twice as many pins as *single-ended* signaling right?
  - wrong! 1.3-1.8x
  - differential signaling has a separate return for each signal
  - typically have 1 return for 2-8 signals





EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

18
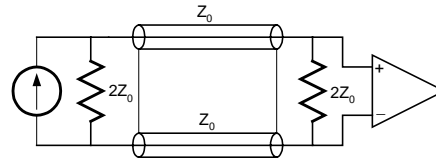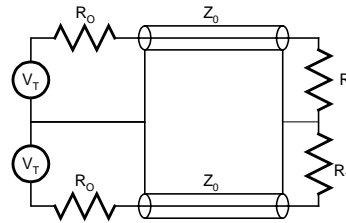
## Advantages of Differential Signaling

- Signal serves as its own reference
  - compare positive signal to complement to detect
- Twice the signal swing
  - effective swing is A-B
- Noise immunity
  - many noise source become common mode
- Return current
  - becomes strictly DC
  - can be 0 for bipolar signaling





EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

19
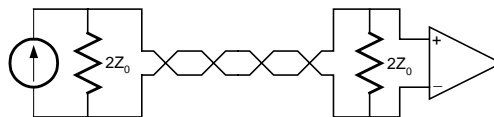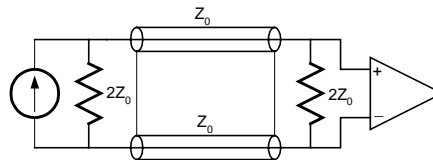
## Differential Signaling and Balanced Transmission Lines



EE273, L7, Oct 14, 1998

Copyright (C) by William J. Dally, All Rights Reserved

20

## Next Time

---

- Signaling over lumped media
  - on-chip capacitive lines
  - off-chip LC circuits
- Signal encoding and Signal Amplitude
- Driving RC lines