

---

## EE273 Lecture 8

# Signaling over Lumped Media

October 19, 1998

William J. Dally  
Computer Systems Laboratory  
Stanford University  
billd@csl.stanford.edu

## Today's Assignment

---

- Reading
  - Sections 8.1 through 8.4
  - Complete before class on Wednesday
- Reminder
  - midterm is in the evening on 10/26
  - no class on 10/26

## A Quick Overview

- Signaling over Capacitive Media
  - Want fast transitions and low power
  - Need to avoid supply noise
  - Current-mode signaling
  - References and Differential signaling
  - Pulsed signaling to avoid DC power dissipation
- Signaling over LRC Interconnect
  - Pin inductance and load capacitance form a tank circuit
  - Adding resistance dampens the oscillation of the tank
  - Slowing rise time reduces excitation
- Number of signal levels
  - trade off bandwidth against noise

EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

3


## Signaling Over Capacitive Media

- Where do we find capacitive wires?
  - short on-chip wires with high fan-out or fan-in
    - e.g. buses, register files, RAMs
    - note that long on-chip wires are RC lines - a more difficult problem
- Desiderata
  - fast transitions
  - low power
  - these imply a small signal swing
  - to support a small swing one needs to isolate power supply noise

EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved



4

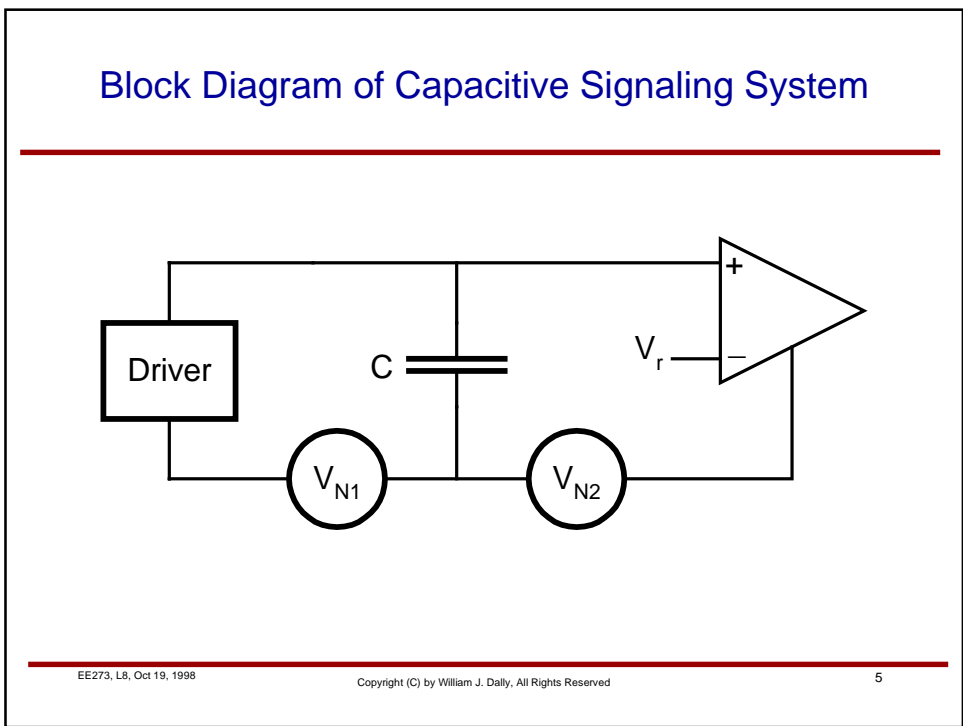
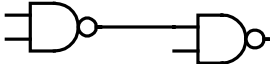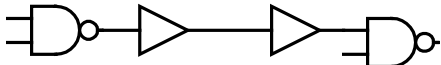
### Conventional *Logic* Signaling

---

- Historically signal levels were defined to facilitate *logic circuits* not *transmission*
  - for example:
    - $0 = \text{TGND}, 1 = \text{TVDD}$
    - $V_r = (\text{RGND} + \text{RVDD})/2$
    - slow
    - lots of power dissipation
    - no rejection of supply noise
- When transmission is a large fraction of delay, its better to switch to a representation tailored for transmission





---

EE273, L8, Oct 19, 1998 Copyright (C) by William J. Dally, All Rights Reserved 6
 
## Current-Mode Signaling

- Send logic values as small currents
  - 1=1mA
  - 0=0mA
- Detect across 'resistor' at receiver
- High Tx impedance isolates Tx supply noise
- High-pass RC removes low-frequency Rx supply noise
- Still need to generate a reference




EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

7

## A Current-Mode Signaling Circuit

 


EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

8
 
## Another Current-Mode Signaling Circuit Negative Feedback Current Sense




EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

9
 
## Transmitter References

- Would like to set receiver reference half-way between a '1' and a '0'
- Simplest approach is to send half the '1' current from the transmitter
  - this reference can be shared by many signals
- If drive current is 1mA, signal swing is 0.3V, and capacitance is 10pF, what is the rise time?
  - how does it depend on signal swing?




EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

10
 
## Differential Signaling

- If wire tracks are available, best noise cancellation is to send the signal and its complement
  - *twist* the signals periodically to balance crosstalk
  - better noise rejection
  - balanced load on the two lines
  - twice the signal swing for the same current (or half the rise time)
- But this still dissipates DC power!




EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

11
 
## Pulsed Signaling

- To eliminate DC power dissipation just
  - (1) remove the 'resistors'
  - (2) drive the line with current pulses
- What does (1) do to noise rejection?
- How do we set the DC level of the line?
  - precharge
  - feedback
- Do we need to pulse the line in both directions?




EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

12
 
## Case Study, SRAM Bit Lines

- SRAMs have high fan-out on the word lines and high fan-in on the bit lines
- Bit lines use differential, pulsed, precharged current-mode signaling
- Typically have 50mV to 300mV swing
  - careful ground rules to make all crosstalk common mode
- Detected with clocked amplifier 10mV offset+sensitivity



EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

13

## SRAM Numbers

- Typical *subarray*
  - 256 rows x 1024 columns
  - 0.5pF bit line, 2pF word line
  - on-current is 0.2mA
  - pulse width is 500ps

$$\Delta V = \frac{I\Delta t}{C} = \frac{(2 \times 10^{-4})(5 \times 10^{-10})}{5 \times 10^{-13}} = 200\text{mV}$$

- How long would it take to go full-swing?

EE273, L8, Oct 19, 1998

Copyright (C) by William J. Dally, All Rights Reserved

14

### SRAM Waveforms

---

---

EE273, L8, Oct 19, 1998
Copyright (C) by William J. Dally, All Rights Reserved
15

### Signaling over LRC Interconnect Or how not to excite the oscillator

---

- Short off-chip wires often look like LC tank circuits
  - inductance of package and bond wire
  - capacitance of load device
  - long off-chip wires look like transmission lines
- Add series or parallel resistance to dampen the oscillations
- Increase the rise time to avoid pumping energy into the LC

$$\omega_0 = (LC)^{-1/2}$$



$$Q = \frac{1}{\pi R_o} \sqrt{\frac{L}{C}}$$

$$K_r = \frac{1}{\omega_0 t_r}$$

---

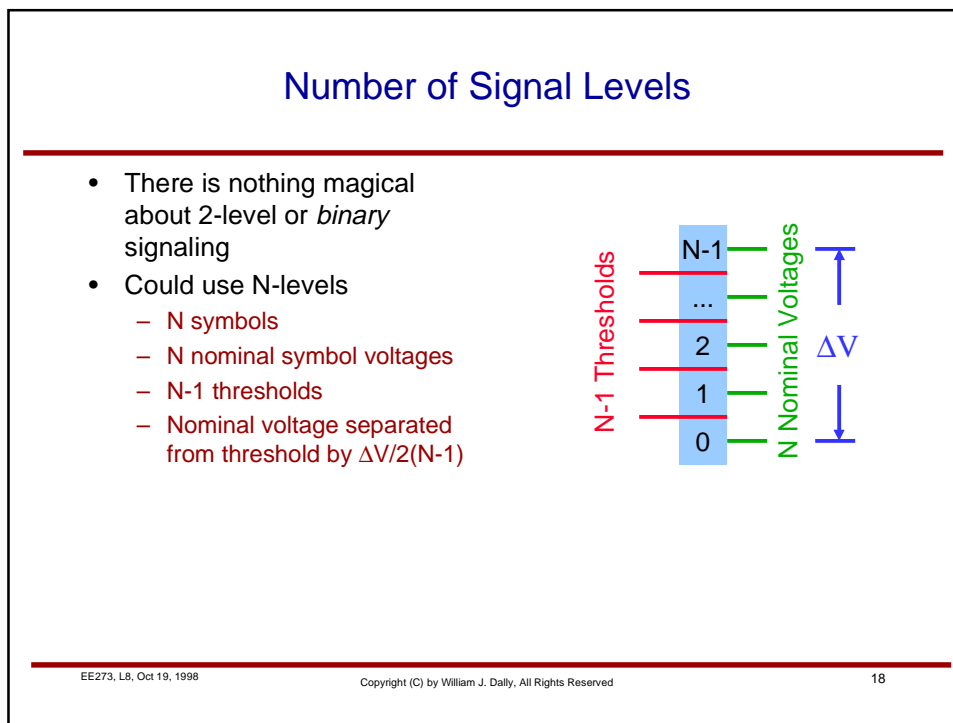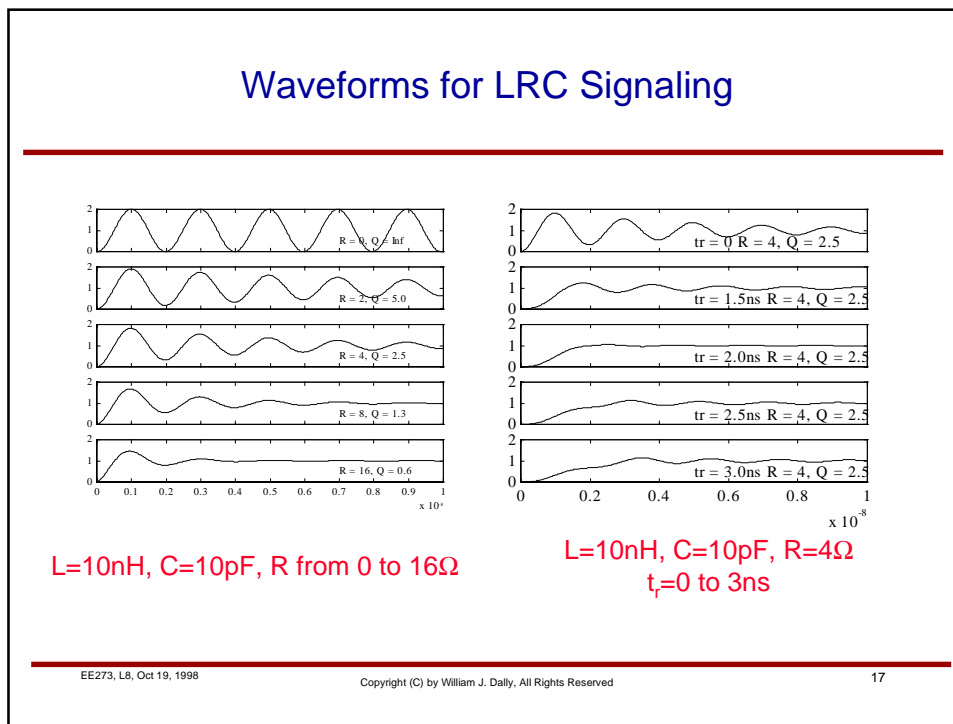
EE273, L8, Oct 19, 1998
Copyright (C) by William J. Dally, All Rights Reserved
16




 
### Multi-Level Signals and Noise

- In the worst case, signal can swing through  $\Delta V$ , from 0 to N-1
  - proportional noise is proportional to full swing
- Gross margin is distance from nominal voltage to threshold
- Proportional noise constant,  $K_N$  must be kept very small to allow more signaling levels
- Number of bits per symbol is  $\log_2(N)$



$$V_{GM} = \frac{\Delta V}{2(N-1)}$$

$$K_N \leq \frac{1}{2(N-1)}$$

### Multi-Level Signals and Power

- Power per symbol (worst case) is proportional to  $\Delta V^2$
- With fixed noise sources this grows as  $N^2$ .
- So power per bit grows as
 
$$\frac{N^2}{\log_2 N}$$
- So why use multilevel signaling?
  - when channel is band-limited
    - it may be the *only* way to get more bits over a channel
  - when there is a very large SNR
    - so proportional noise doesn't swamp the multi-level signal.

## Next Time

---

- Signaling wrapup
- Dealing with long on-chip RC lines
- Dealing with lossy LRC lines
- Simultaneous bidirectional signaling