

---

# EE273 Lecture 2

## Wires

January 17, 2001

William J. Dally  
Computer Systems Laboratory  
Stanford University

# Today's Assignment

---

- Reading
  - Sections 3.4, 3.6, and 3.7
  - Complete before class on Monday 1/22
- Problem set 2
  - Problems 3-8, 3-11, and 3-16 (but with new waveform see web page)
  - Due at start of class on Wednesday 1/24

# Announcements

---

- Book
- Graders


# Outline

---

- Electrical properties of wires
- Equivalent model of an ideal transmission line
- Derivation of the Telegrapher's equation
- Lossy lines
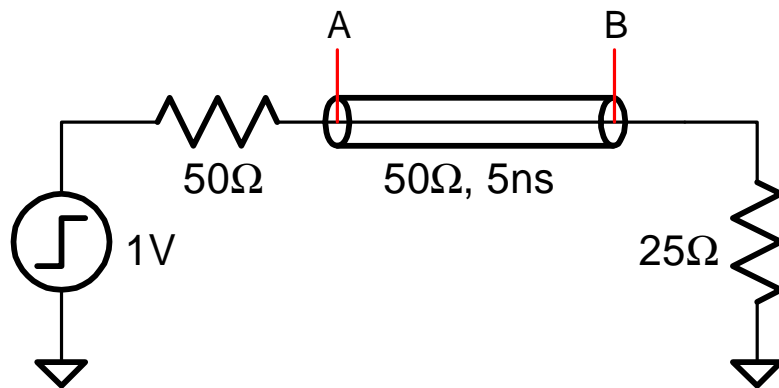
# Last Time

- Three rules of transmission lines
  - Waves propagate down the line (in both directions)
  - Waves reflect unless terminated
  - The voltage on the line is the *superposition* of these waves




$$k_r = \frac{Z_T - Z_0}{Z_T + Z_0} =$$
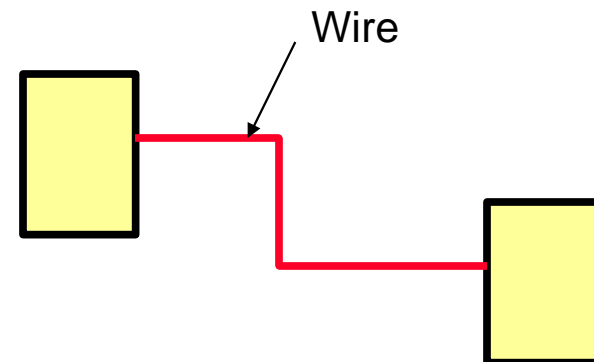
# Wires in Digital Systems


---

- Physically wires are
  - Microstrip and stripline on printed-circuit cards and backplanes
  - Conductors in cables, cable assemblies
  - Connectors
- We tend to treat them as *ideal wires*
  - no delay (equipotential)
  - no capacitance, inductance, or resistance
- They are *not* ideal
- To build reliable systems we need to understand their properties and behavior


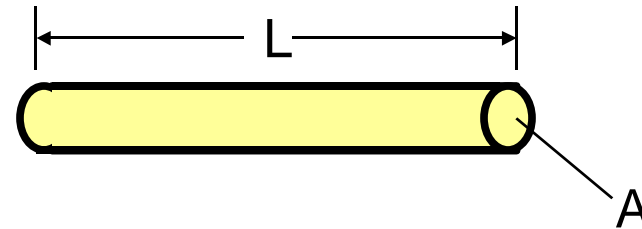
# Resistance of Wires

- Most *real* wires have resistance
- Depends on
  - material (resistivity)
  - length
  - cross section
- Causes
  - delay
  - loss



$$R = \frac{rL}{A}$$

Material	$\rho$ (n $\Omega$ -m)
Ag	16
Cu	17
Au	22
Al	27



# Capacitance of Wires

- Real wires have capacitance

- line charge
- parallel plate
- fringing


- To compute

- assume Q
- compute E field
- integrate to get V


- Think of the energy stored in the E field


$$C = \frac{Q}{V}$$


$$E = \frac{Q}{2\pi r}$$

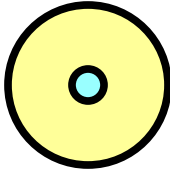


$$C = \frac{2pe}{\log\left(\frac{r_o}{r_i}\right)}$$


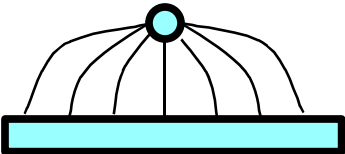
$$C = \frac{2pe}{\log\left(\frac{s}{r}\right)}$$



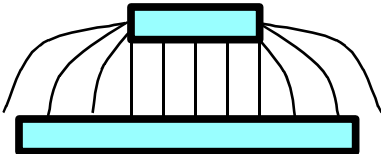
$$\frac{2pe}{\log\left(\frac{2s}{r}\right)}$$



$$C = \frac{we}{d} + \frac{2pe}{\log\left(\frac{2s}{r}\right)}$$

# Inductance of Wires


- Real wires have inductance

$$L = \frac{\mathbf{f}}{I}$$

- In a homogenous medium

$$CL = \mathbf{em}$$

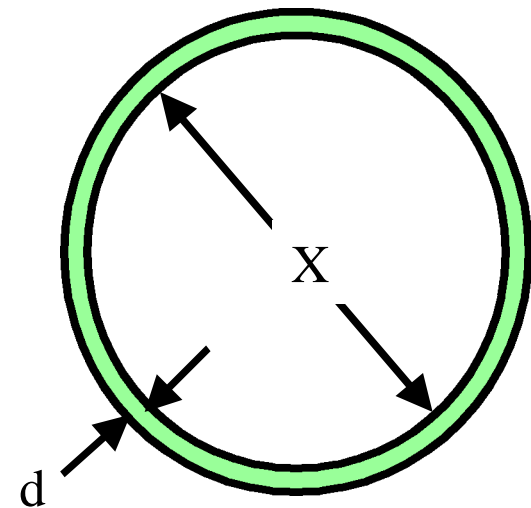- Inductance is a purely geometric property of a **closed** circuit
- Think of the energy stored in the magnetic field



$$L = 3.96 \cdot 10^{-10} X \left( \ln \left[ \frac{8X}{d} \right] - 2 \right)$$

## Some Example Wires

---

Type	W	R	C	L
On chip	0.6 $\mu\text{m}$	150k $\Omega/\text{m}$	200pf/m	600nH/m
PC Board	150 $\mu\text{m}$	5 $\Omega/\text{m}$	100pf/m	300nH/m
24AWG pair	511 $\mu\text{m}$	0.08 $\Omega/\text{m}$	40pf/m	400nH/m

Scale model of a line has different R, but same L and C per unit length

# Qualitative L and C


---




$$L = L_1, \quad C = C_1, \quad R = R_1$$


 
$$L = \quad, \quad C = \quad, \quad R = \quad$$


 
$$L = \quad, \quad C = \quad, \quad R = \quad$$




$$L = \quad, \quad C = \quad, \quad R = \quad$$

# Wire Models


- In a particular situation, we create a *model* of a wire that captures the properties we need
  - ideal
  - lumped L, R, or C
  - RC transmission line
  - LC transmission line
  - General LRCG transmission line
- Model to use depends on frequency

$$f_0 = \frac{R}{2pL}$$

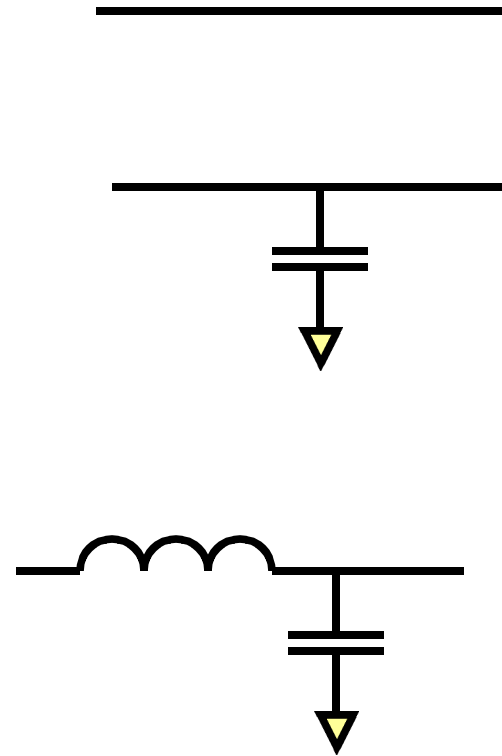

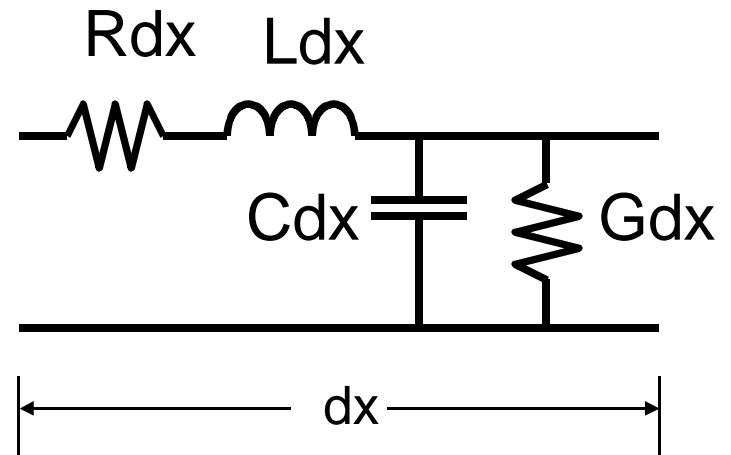
# LRCG Wire Model

- Model an *infinitesimal* length of wire,  $dx$ , with lumped components
  - L, R, C, and G



# Transmission Line Equations

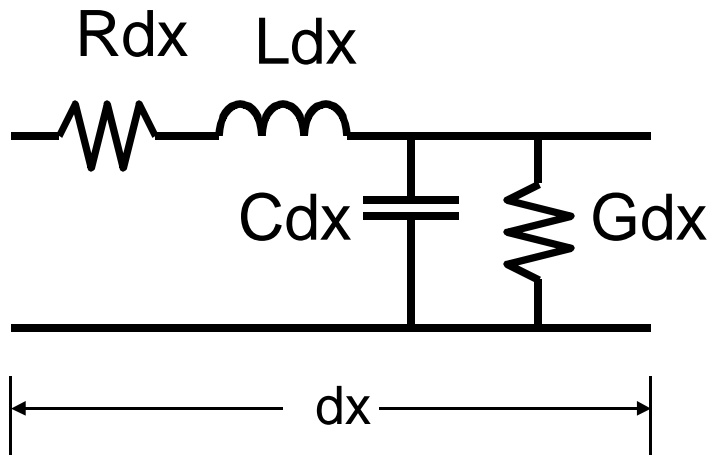

Drop across R and L

$$\frac{\partial V}{\partial x} = RI + L \frac{\partial I}{\partial t}$$

Current into C and G

$$\frac{\partial I}{\partial x} = GV + C \frac{\partial V}{\partial t}$$

$$\frac{\partial^2 V}{\partial x^2} = RGV + (RC + LG) \frac{\partial V}{\partial t} + LC \frac{\partial^2 V}{\partial t^2}$$


# Solving this equation gives us two key properties of the line

---

- Impedance
  - I-V relationship at terminal
- Propagation constant
  - How a signal propagates down the line
    - How fast
    - How much distortion
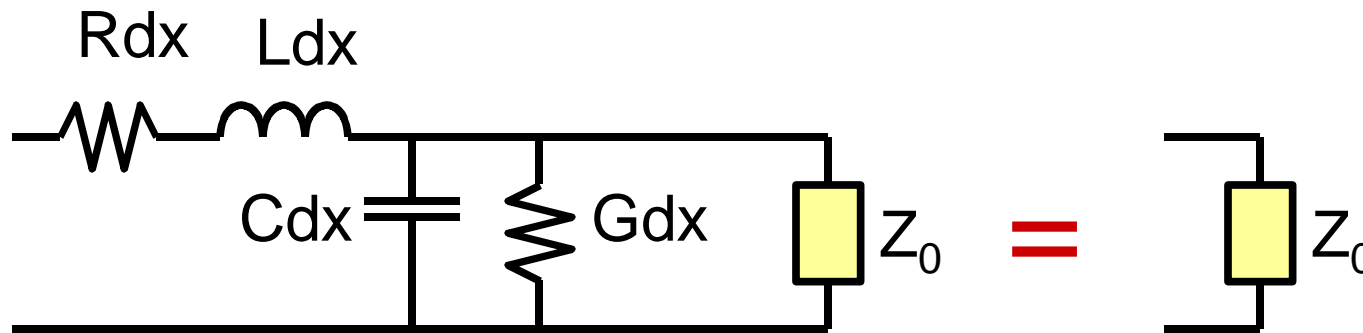
# Impedance

- An infinite length of LRCG transmission line has an *impedance*  $Z_0$
- Driving a line *terminated* into  $Z_0$  is the same as driving  $Z_0$
- In general  $Z_0$  is complex and frequency dependent
- For LC lines its real and independent of frequency



$$Z_0 = \left( \frac{R + Ls}{G + Cs} \right)^{\frac{1}{2}}$$


$$Z_0 = \left( \frac{L}{C} \right)^{\frac{1}{2}}$$

At high frequency (LC lines)
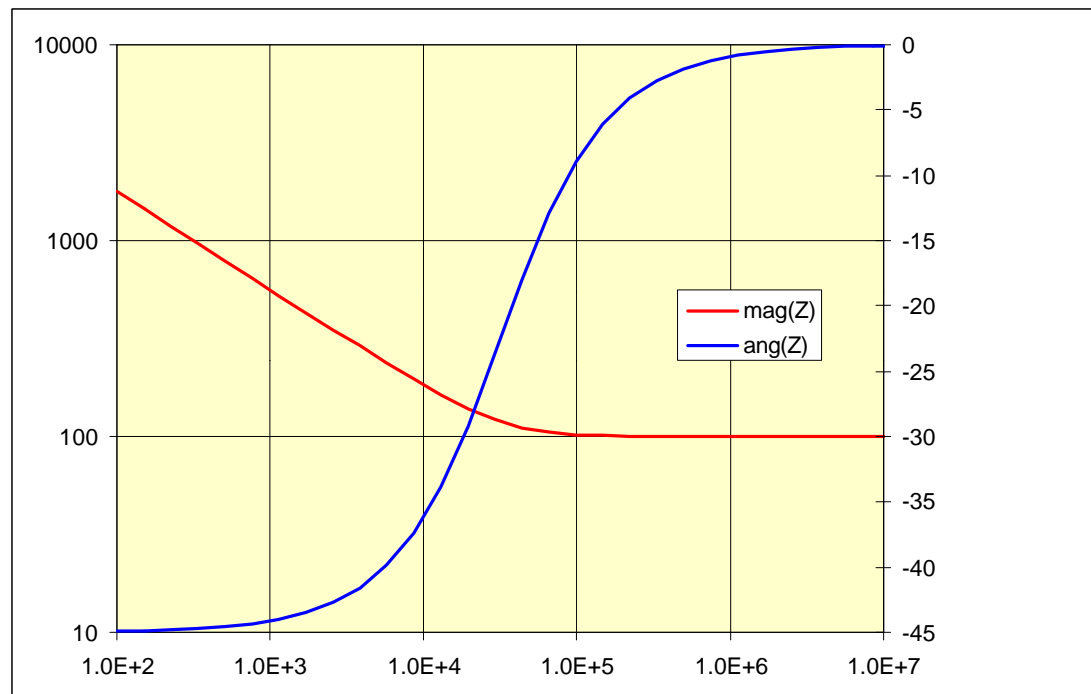
## Example, 24AWG Pair

- $f_0 = 33\text{kHz}$
- Below  $f_0$ , line is RC
- Above  $f_0$ , line is LC


$$Z_0 = \left( \frac{.08 + 400 \times 10^{-9} \times 2pfj}{40 \times 10^{-9} \times 2pfj} \right)^{\frac{1}{2}}$$


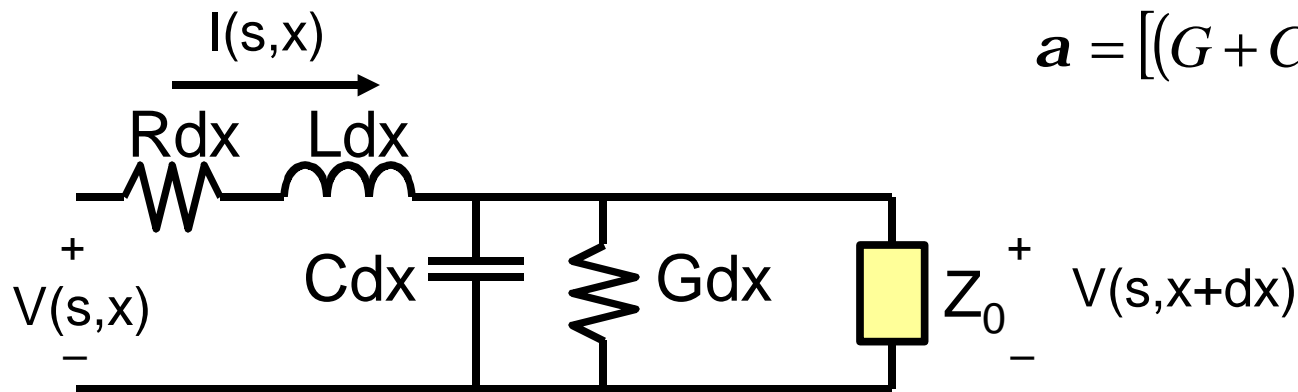
# Propagation Constant

- Using impedance, we can solve for  $V(s,x)$
- Propagation is governed by a constant,  $\alpha$ 
  - real part is attenuation
  - imaginary part is phase shift
    - velocity<sup>-1</sup>
    - $v = (LC)^{-1/2}$

$$\begin{aligned} \frac{\partial V(s)}{\partial x} &= -(R + Ls)I(s) \\ &= -(R + Ls)V(s)/Z_0 \\ &= -[(G + Cs)(R + Ls)]^{1/2} V(s) \\ V(s, x) &= V(s, 0) \exp(-\mathbf{a}x) \\ &= V(s, 0) \exp(-\mathbf{a}_{RE}x) \exp(-\mathbf{a}_{IM}x) \\ \mathbf{a} &= [(G + Cs)(R + Ls)]^{1/2} \end{aligned}$$



# Lossless LC Lines

- If R and G are negligible
  - line is lossless (no dissipation)
  - governed by the *wave equation*
- Waves propagate down the line in both directions without distortion
- Line is described by its ***impedance*** and ***velocity***
- For a general LCRG line we have ***impedance*** and ***propagation constant***

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$



$$V_f(x, t) = V\left(0, t - \frac{x}{v}\right)$$

$$V_r(x, t) = V\left(x_{\max}, t - \frac{x_{\max} - x}{v}\right)$$

$$v = (LC)^{-\frac{1}{2}}$$



$$Z_0 = \left(\frac{L}{C}\right)^{\frac{1}{2}}$$

# Driving a Line - Equivalent Circuit

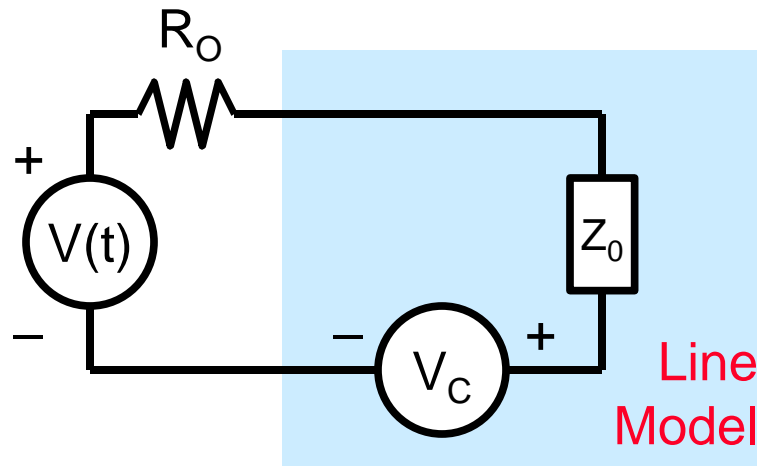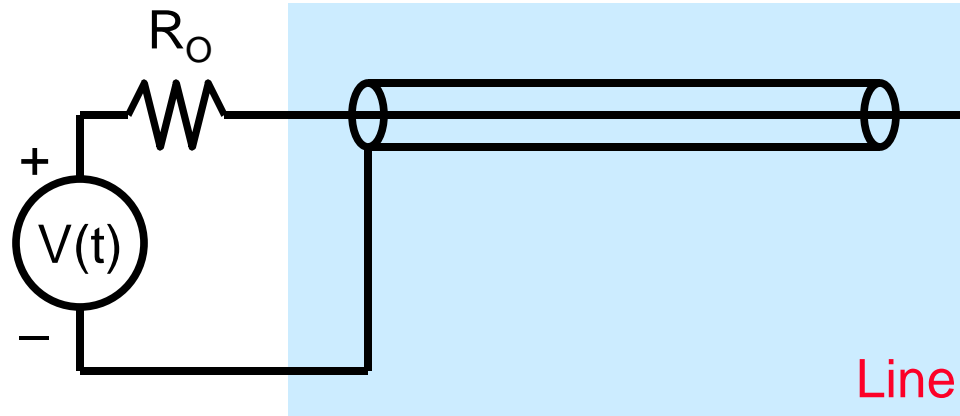


Response of line to voltage source depends on previous state of line,  $V_c$

# Termination - Equivalent Circuit

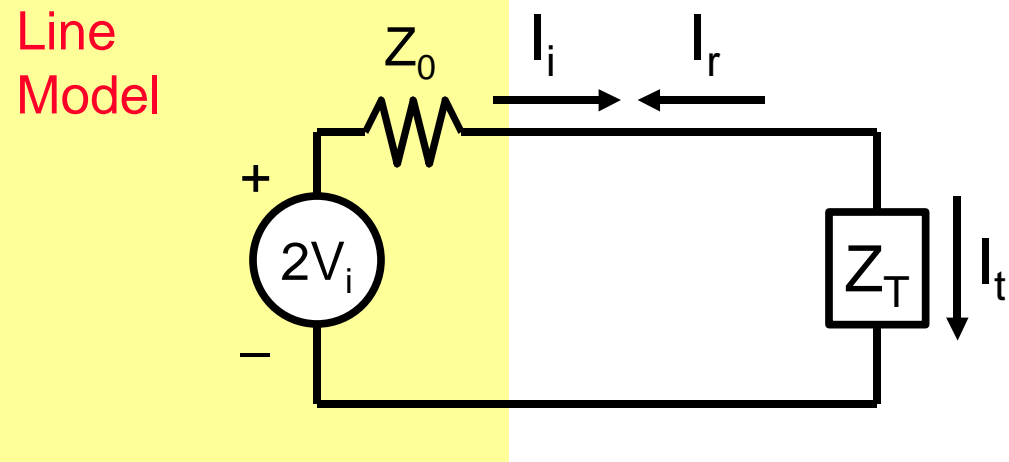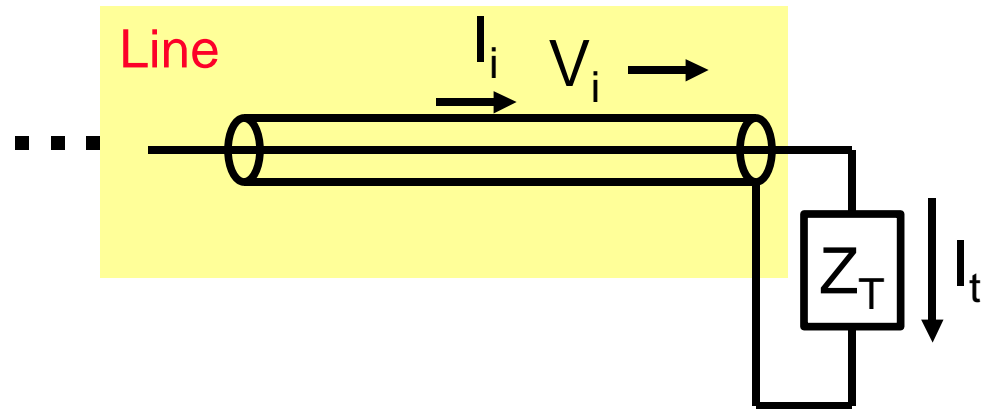
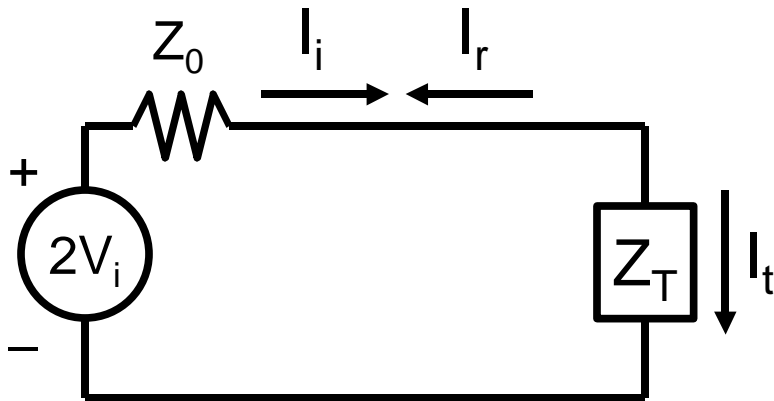
# Reflections and The Telegrapher's Equation

- Incident wave determines  $V_i$ ,  $I_i$
- Use equivalent circuit to solve for  $V_T$ ,  $I_T$
- Use superposition to calculate  $V_r$ ,  $I_r$



$$I_T = \frac{2V_i}{Z_0 + Z_T}$$

$$I_r = I_i - I_T$$


$$I_r = \frac{V_i}{Z_0} - \frac{2V_i}{Z_0 + Z_T}$$

$$I_r = \frac{V_i}{Z_0} \left( \frac{Z_T - Z_0}{Z_T + Z_0} \right)$$


$$\frac{I_r}{I_i} = \frac{V_r}{V_i} = \left( \frac{Z_T - Z_0}{Z_T + Z_0} \right)$$
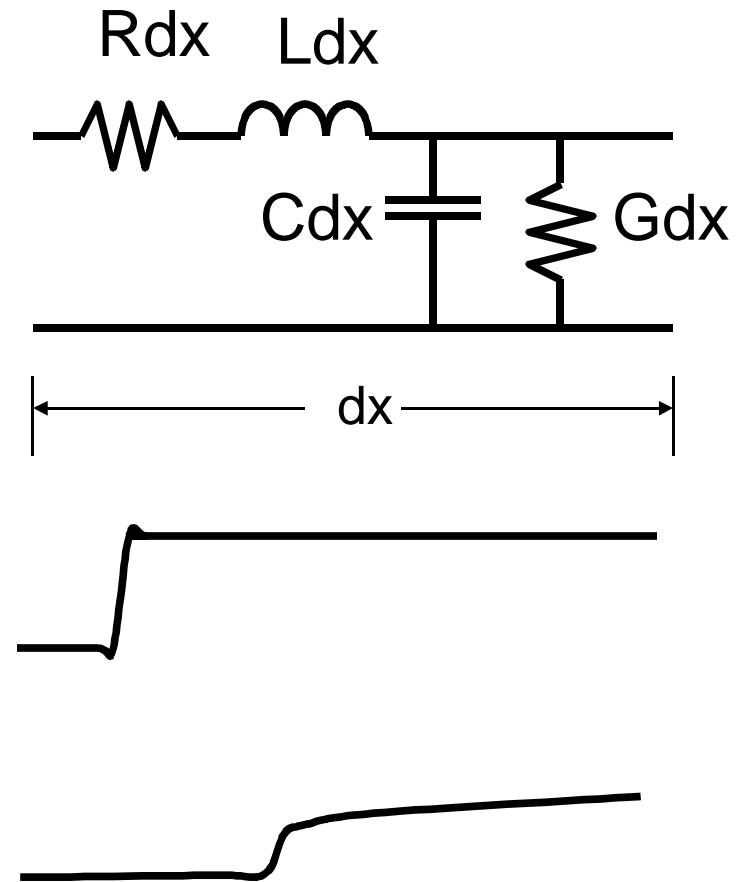
# Lossy Transmission Lines

- LC lines with resistance and conductance
  - propagation mostly by wave
  - some by diffusion
- R and G dissipation
  - reduces the amplitude of the signal
  - disperses the signal
    - fast rise to AC attenuation
    - slow tail to DC attenuation
- Resistance and conductance depend on frequency
  - we will ignore this for now



# Zero-th Order Waveform




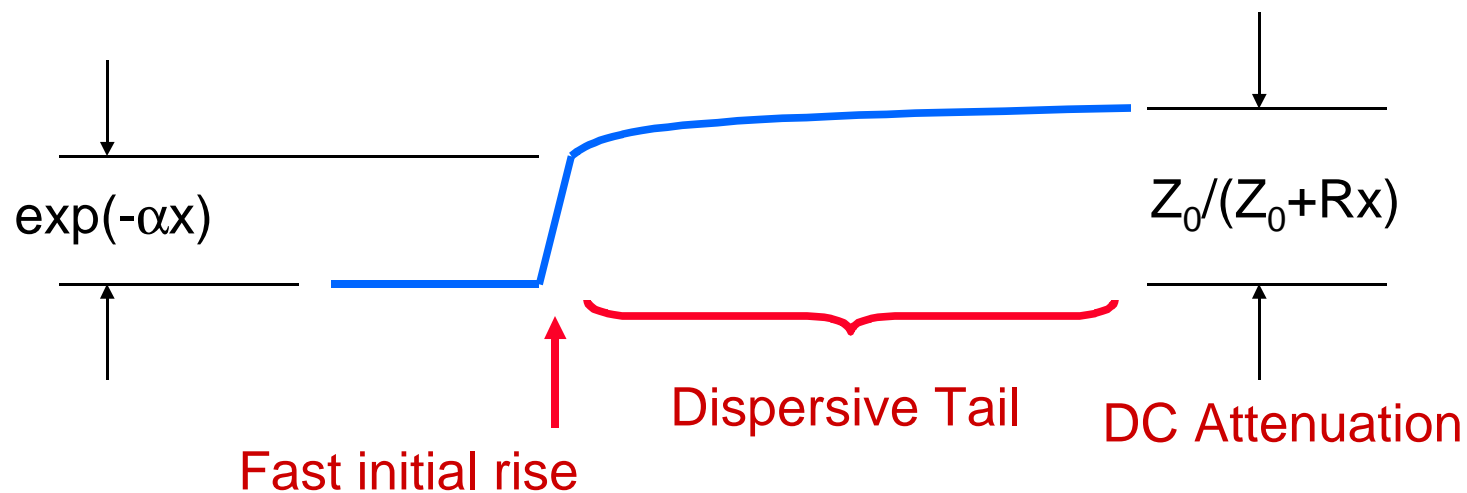


$$a = [(G + Cs)(R + Ls)]^{\frac{1}{2}}$$

Q: So why worry about attenuation?

A: It closes the eye opeing!

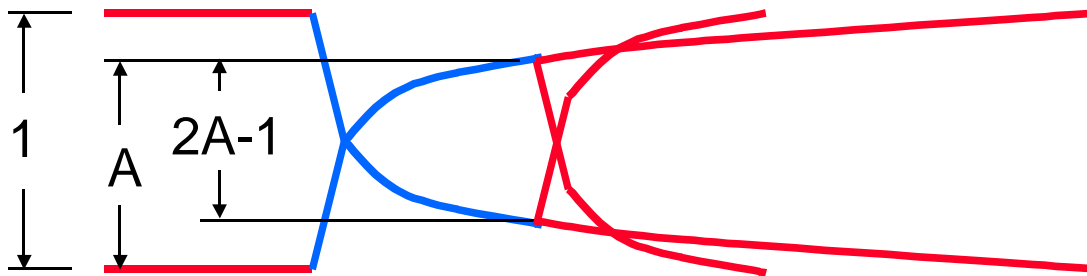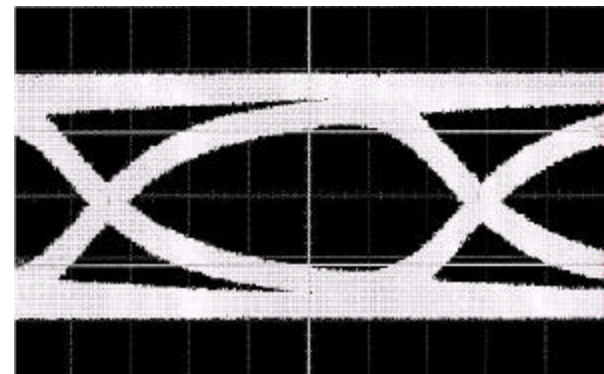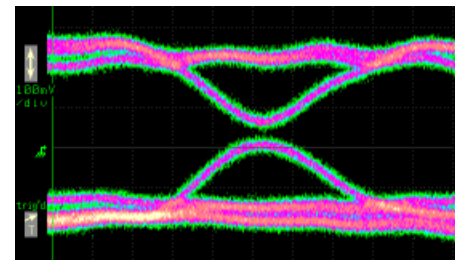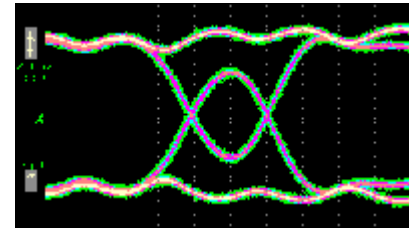
- Critical parameter is what fraction of swing,  $A$  is achieved in one bit time
- Eye opening is reduced to  $B = 2A - 1$
- No eye opening at 50% attenuation
- Significant degradation of margins at lower levels of attenuation



# Skin Effect Resistance

- Beauty is only skin deep - so is current
  - current density drops off exponentially with depth
- Skin depth decreases with frequency,  $f^{-1/2}$
- Model as if all current flowed in  $\delta$ -thick outer layer of conductor

$$d = (pfms)^{-1/2}$$

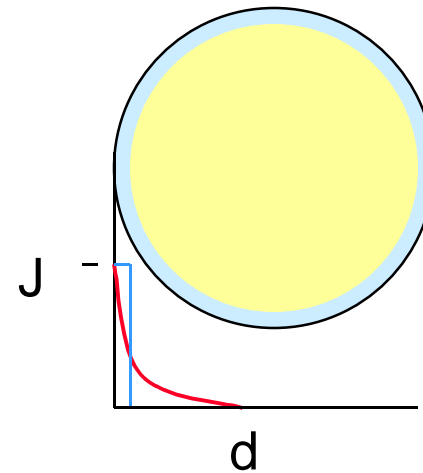

$$J = \exp\left(-\frac{d}{d}\right)$$


# Skin-Effect Resistance

---

- Effect does not occur until frequency,  $f_s$ , at which skin depth equals conductor radius
- Above  $f_s$ ,  $R$  and  $A$  increase as the square-root of frequency

$$R(f) = \frac{R_{DC}}{2} \left( \frac{f}{f_s} \right)$$
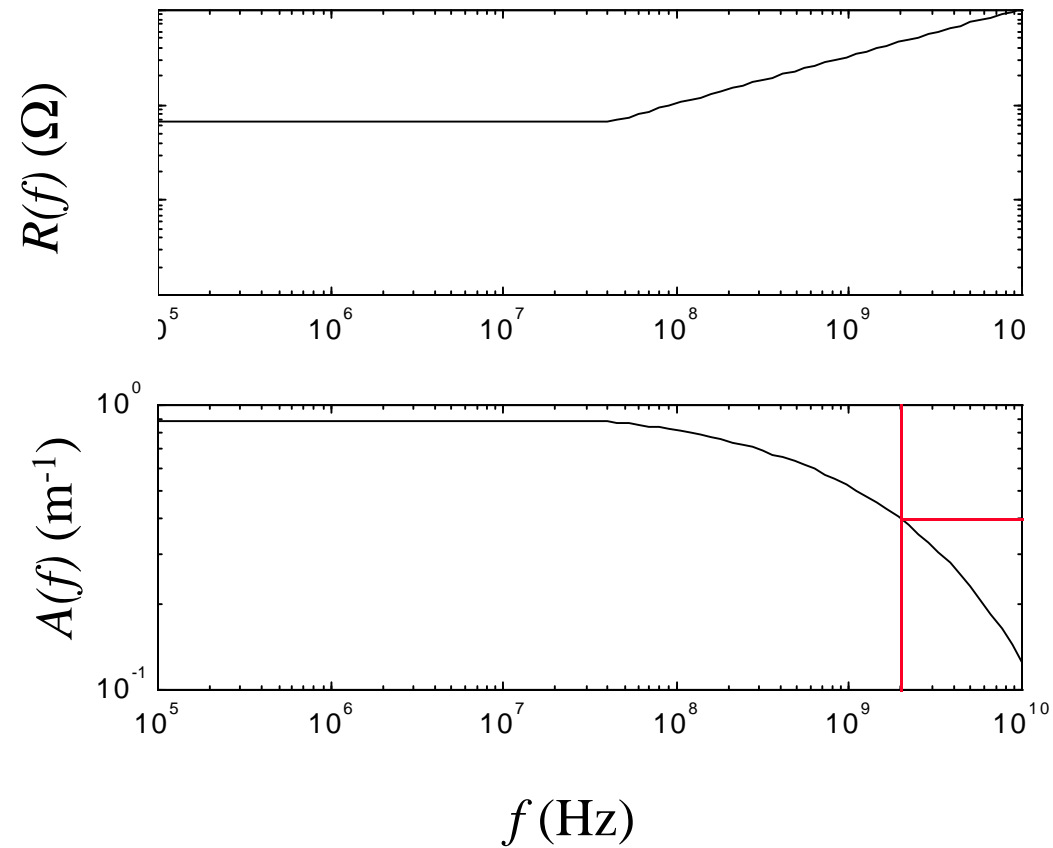
# Resistance and Attenuation of 5mil 0.5oz 50Ω Stripguide



0.40, 8dB/m

# Dielectric Absorption

- High frequency signals *jiggle* molecules in the insulator
  - insulator *absorbs signal energy*
- This effect is approximately linear with frequency and is modeled as a conductance
- Dielectric loss is often specified in terms of a *loss tangent*,  $\tan(\delta)$

$$\tan \mathbf{d} = \frac{G}{\omega C}$$


$$\mathbf{a}_D = \frac{G Z_0}{2}$$

$$= \mathbf{p} f \tan \mathbf{d} \sqrt{LC}$$

$$= \frac{\mathbf{p} \sqrt{\mathbf{e}_r} f \tan \mathbf{d}}{c}$$

material	$\tan \delta$
FR4	0.035
Polyimide	0.025
GETEK	0.010
Teflon	0.001
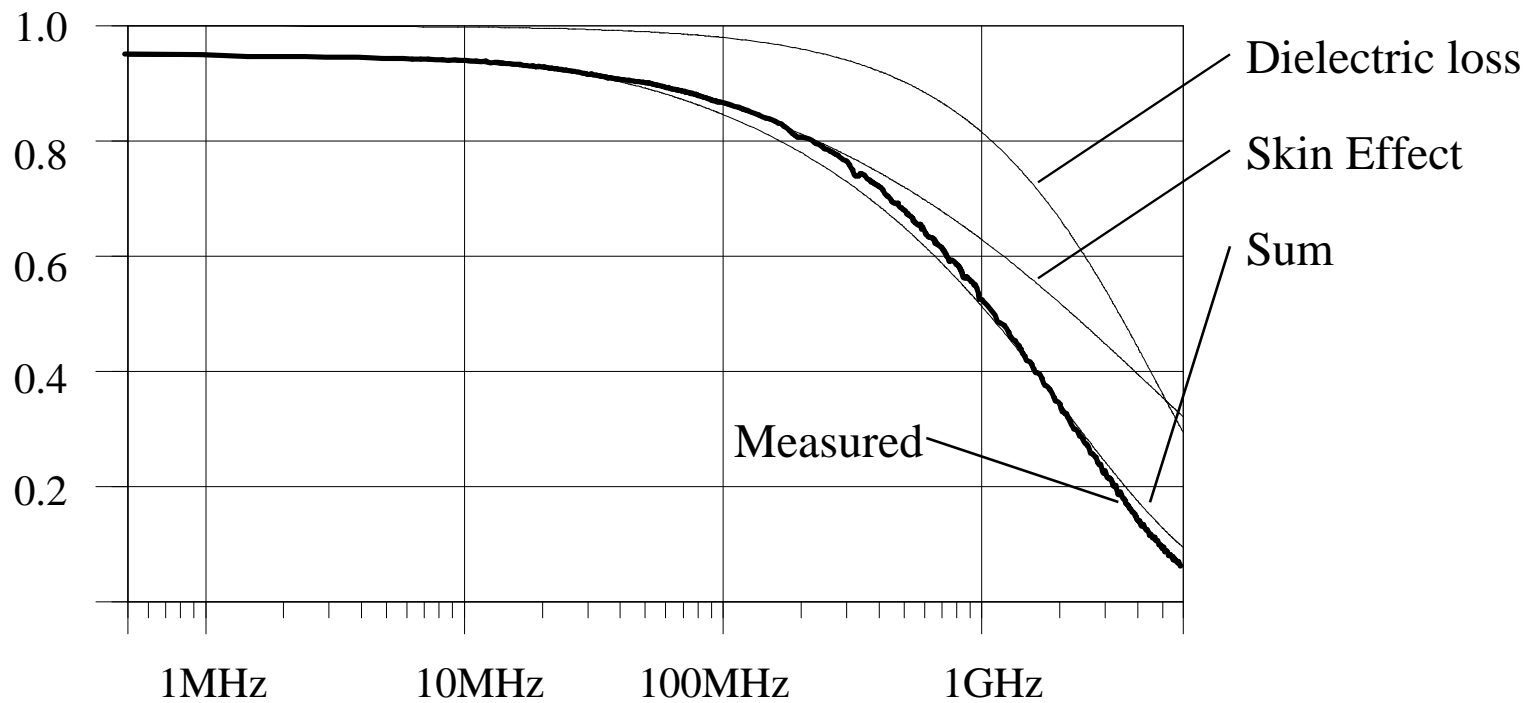
# Skin effect resistance and dielectric absorption



1m 8mil 50Ω stripguide with GETEK dielectric

# The $Bd^2$ Constant

- Suppose you can tolerate a certain attenuation,  $A$ 
  - eye opening is  $2A-1$
- At a certain bandwidth,  $B_1$ , attenuation  $A$  is achieved with a distance of 1m
- As bandwidth is increased, resistance, and hence attenuation, increases as  $B^{1/2}$
- So distance must be decreased by a proportional amount

$$A(B_1) = A_1$$

$$A(B, d) = A_1 d \left( \frac{B}{B_1} \right)^{1/2}$$

$$Bd^2 = B_1$$

Doubling distance cuts  
bandwidth by a factor of 4

## Next Time

---

- Transmission line wrapup
- Differential lines
- Multi-drop buses