
EE273 Lecture 8

Advanced Signaling

February 7, 2001

William J. Dally
Computer Systems Laboratory
Stanford University
billd@csl.stanford.edu

Logistics



- No homework this week
- Demo
 - Friday 2/9/01 12Noon to 12:50PM
 - Gates B03 (Channel E3)
- Midterm
 - Monday 2/12/01 from 7:00PM to 9:00PM
 - Room 200-2
 - We will be having class on Monday
- Reading
 - Sections 9.1 through 9.5
 - Complete before class on Monday 2/12

A Quick Overview

- Driving long RC wires
 - on chip wires are like wet noodles
 - delay and rise time are quadratic with length
 - 80ps/mm² in 0.18μm
 - can make delay linear with repeaters
 - wider wires help a little
 - fringing fields
 - fatter (taller) wires help a lot
- Driving lossy LC lines
 - frequency dependent loss closes the eye diagram
 - a lone pulse is affected the most
 - equalization can cancel the frequency dependent loss
- Simultaneous bidirectional signaling
 - use both forward and reverse traveling wave at the same time

Long On-Chip Wires are Diffusive RC Lines


- Typical wire $0.5\mu\text{m} \times 0.5\mu\text{m}$ Aluminum ($0.35\mu\text{m}$ technology)
 - $R = 120\Omega/\text{mm}$
 - $C = 160\text{fF}/\text{mm}$
 - $\tau = RC = 19\text{ps}/\text{mm}^2$
- Delay *and* Rise Time are **quadratic** with distance
- Complicated by R of wire and C of load
- Large drivers don't help - R of wire dominates
- Problem is getting worse with time
 - $80\text{ps}/\text{mm}^2$ in $0.18\mu\text{m}$ technology

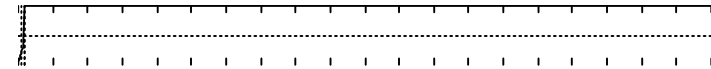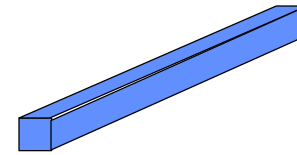

Response of 30mm wire at 5mm intervals

Optimal Repeater Spacing

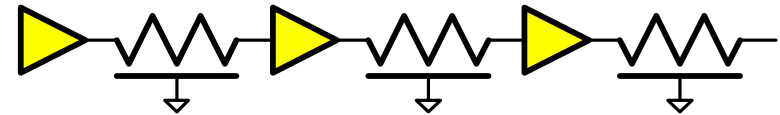- Repeaters convert quadratic delay to linear delay
- Optimal repeater spacing is when the delay of the **repeater** equals the delay of the **wire**
 - about 3mm for an 0.35μm process
 - about 1mm for a 0.18μm process
- Results in a maximum signal propagation velocity that goes as the inverse root of RC (nearly linear with line width)




$$t_d = \left(\frac{l}{l_s} \right) \left(t_b + 0.4 l_s^2 RC \right)$$

$$v = \frac{1.3}{\sqrt{t_b RC}}$$

Optimal Repeater Spacing

The Graph


0.35 μ m technology

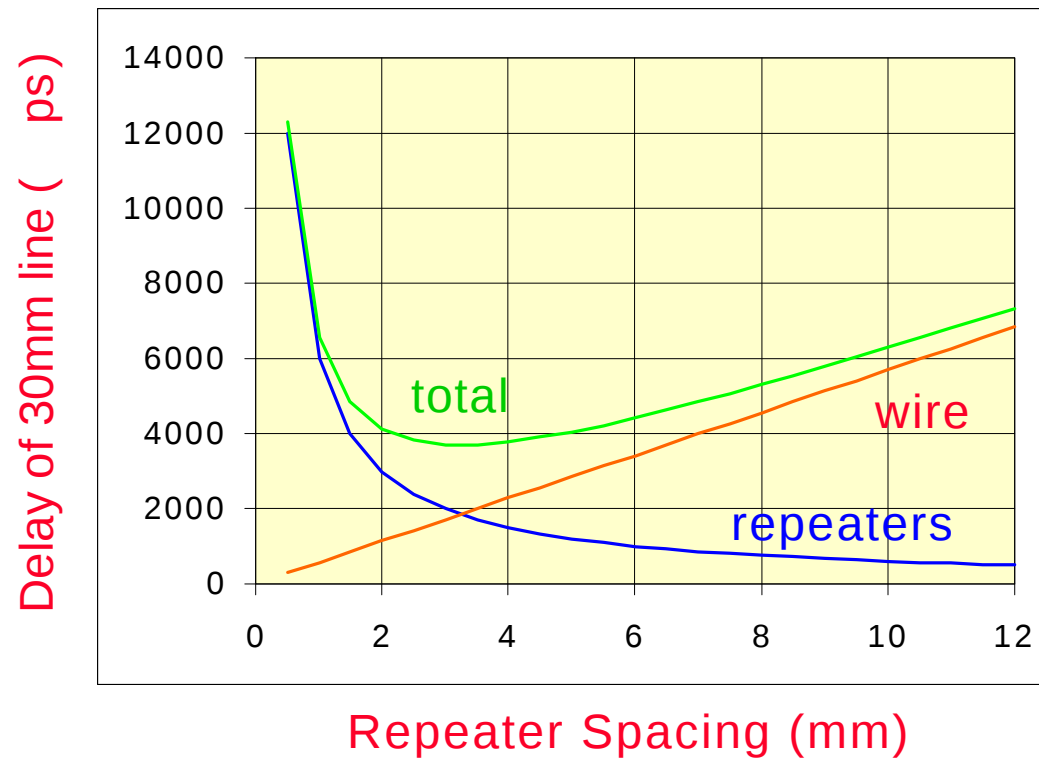



Fat Wires Help (a little)

Thick, Fat Wires Help a lot

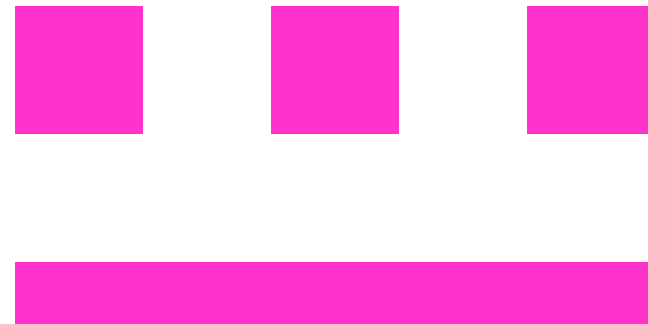- Making wires wider than minimum width doesn't help much
 - R decreases
 - C parallel plate increases
 - C fringing stays the same
- Making wide wires on thick metal layers helps **a lot**
 - R decreases
 - C stays the same
- Can have a few fast wires or lots of slow wires





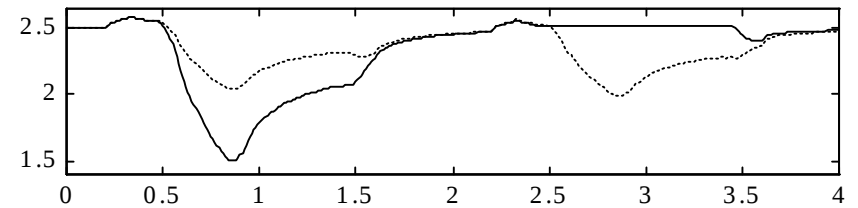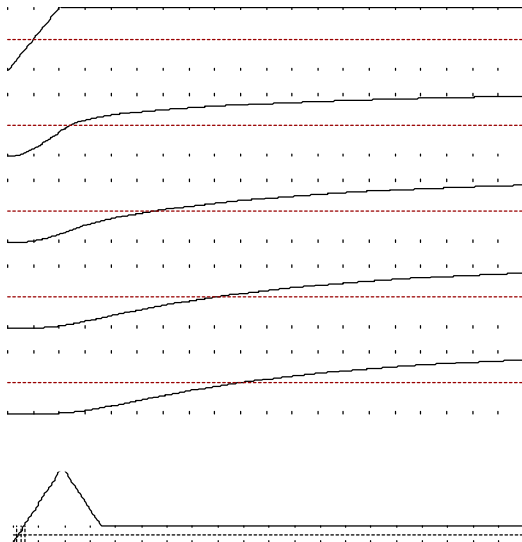Overdrive increases signal velocity by 3x




Long Off-Chip Wires are Lossy LRC Lines

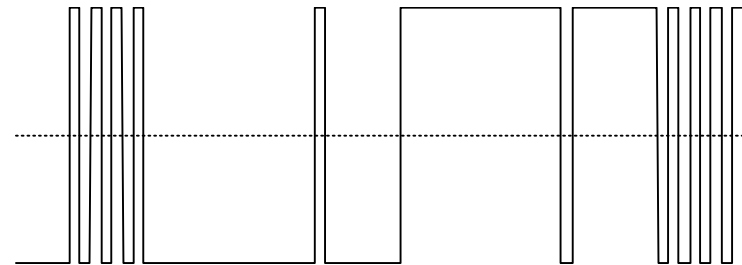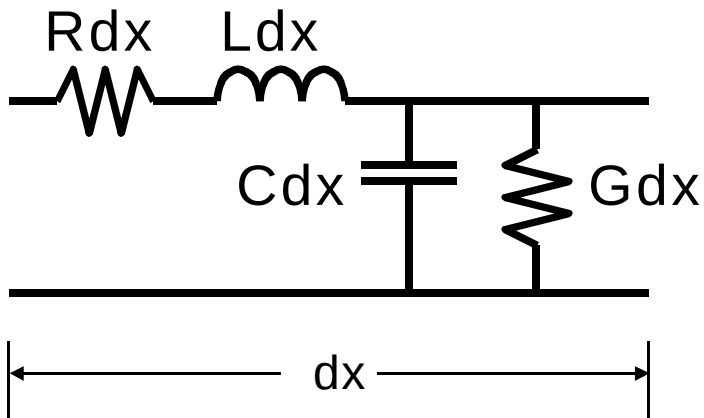- Long off-chip wires are LRC transmission lines
 - fast rise to AC attenuation
 - long diffusive tail
 - complicated by frequency-dependent attenuation due to skin effect



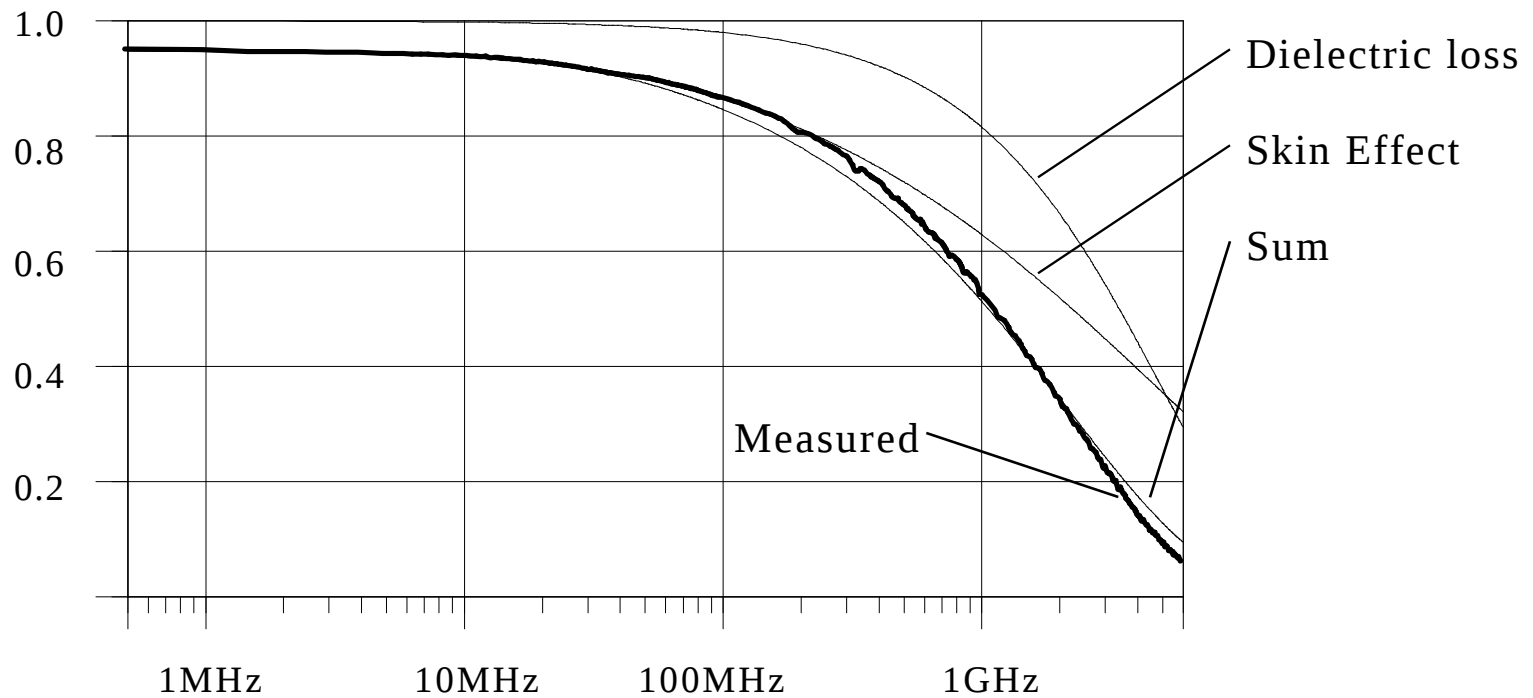
Skin effect resistance and dielectric absorption





1m 8mil 50Ω stripguide with GETEK dielectric

The problem of the '*Lone Pulse*'

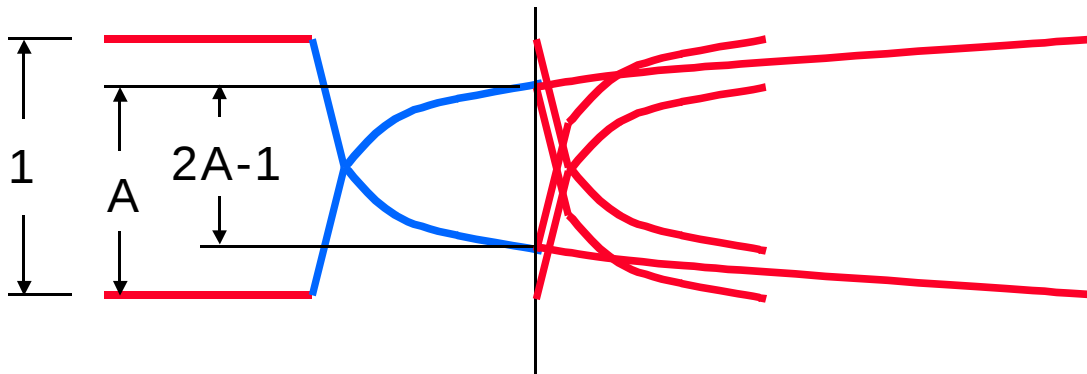- Critical parameter is what fraction of swing, A is achieved in one bit time
- Eye opening is reduced to $B = 2A - 1$
- No eye opening at 50% attenuation
- Also results in data-dependent jitter



With Transmitter Equalization

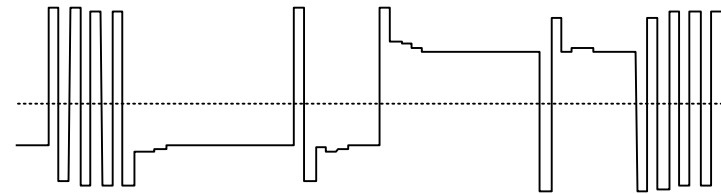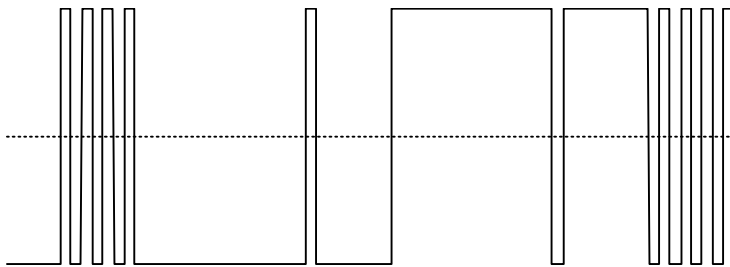


Before



After

Solution - Equalization

1m 5mil
stripguide

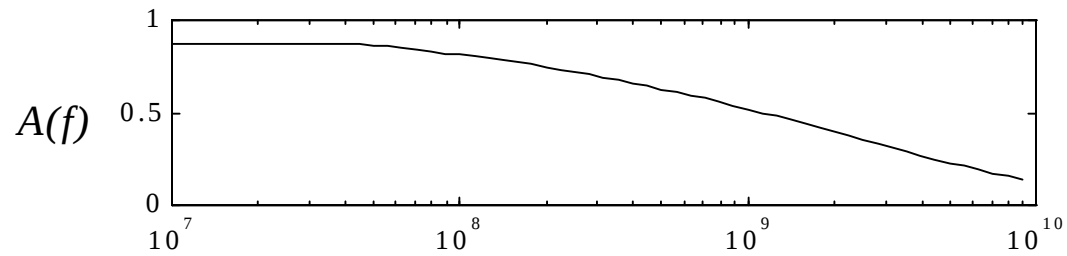

$H(f)$


$A(f)H(f)$



f (Hz)



Equalization - A Simple Implementation

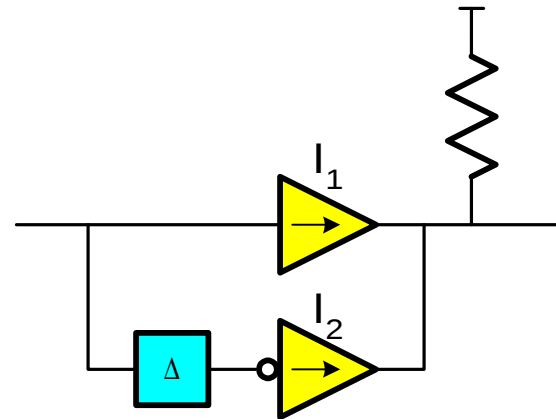- Two-tap FIR filter
 - send AC component (adjacent bits different) at full magnitude
 - send DC component (adjacent bits the same) at reduced magnitude
- Implement with two transmitters
 - one lags the other by one bit and drives in the opposite direction




Equalization




Some Photos

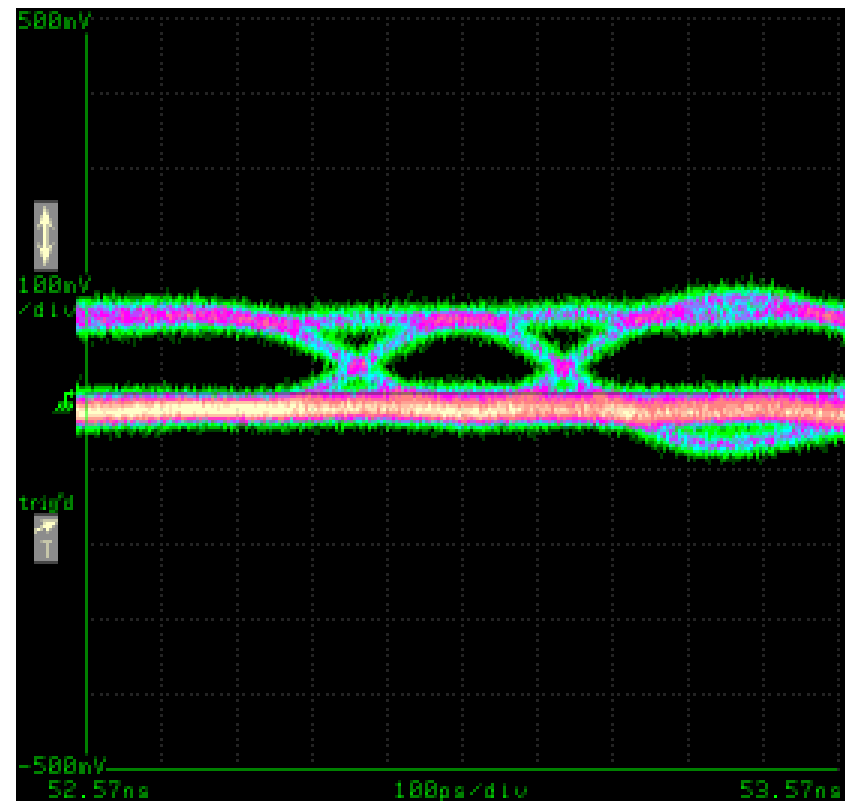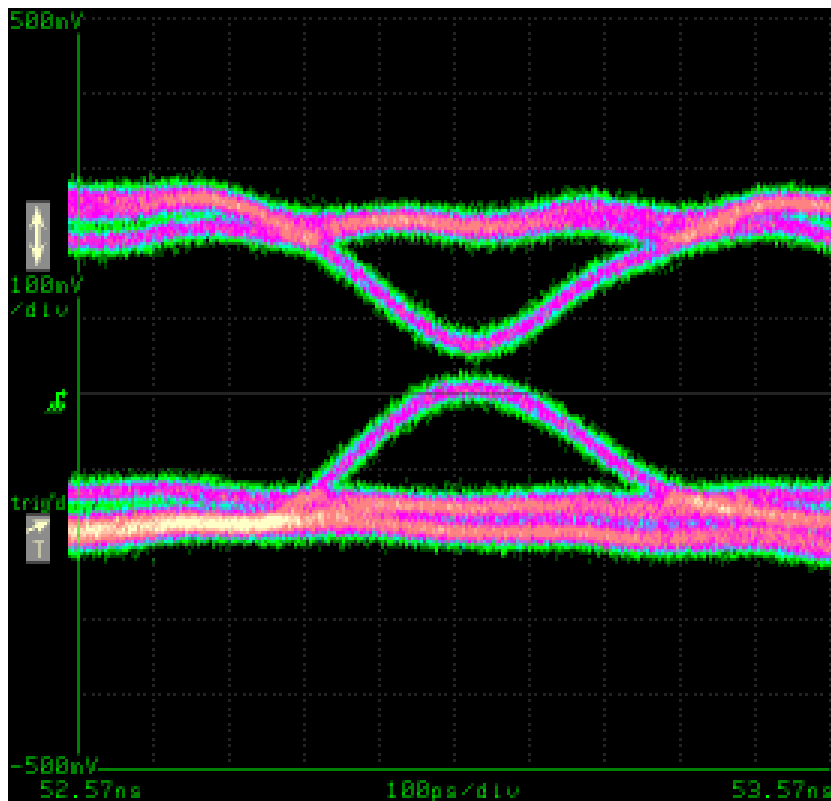

More Pictures

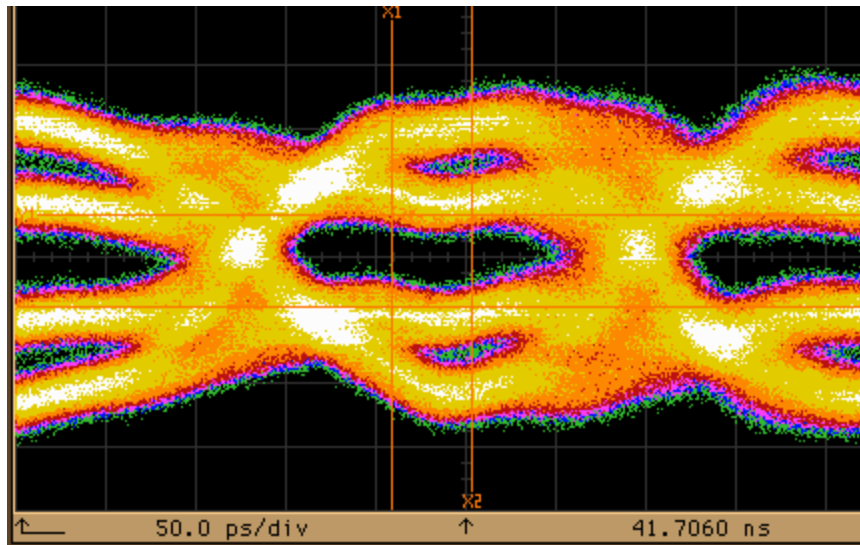

Still More Pictures

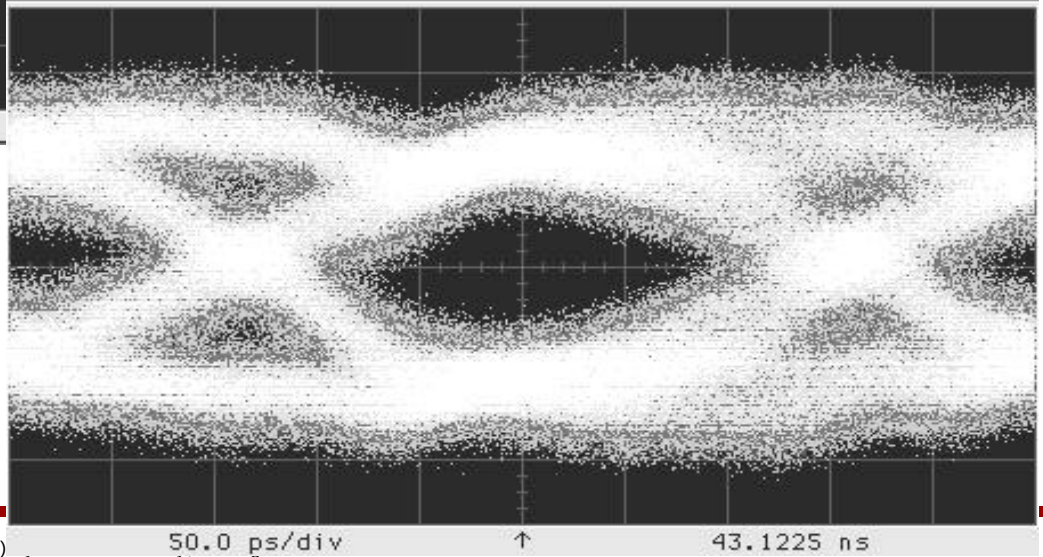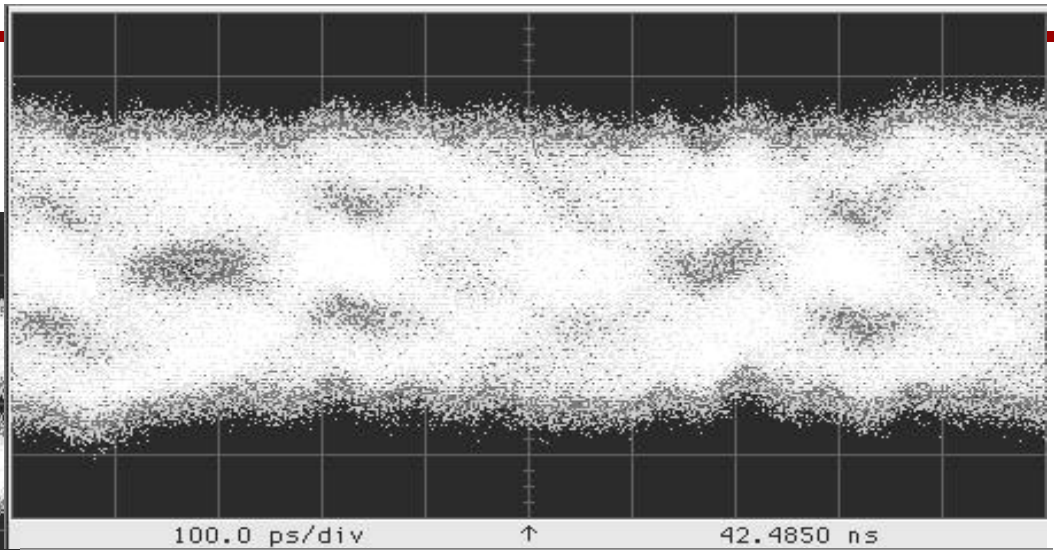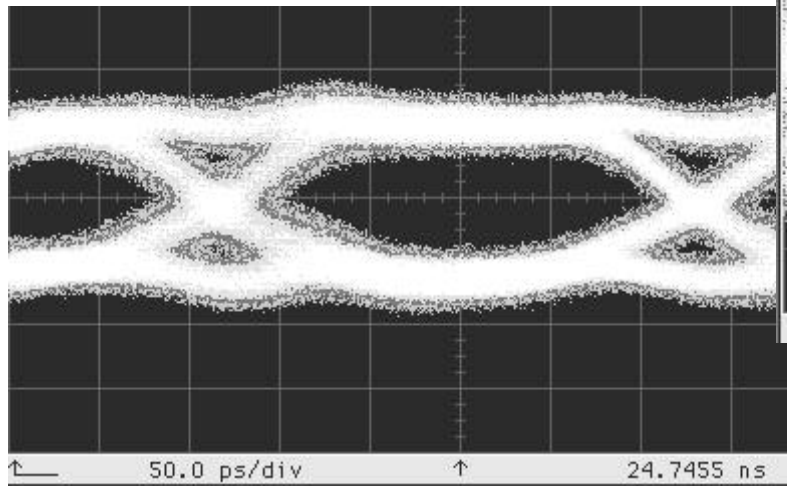


Simultaneous Bidirectional Signaling


- Wires can transmit waves in both directions
- It seems a shame to only use one direction at a time
- Simultaneous bidirectional signaling
 - transmit waves in both directions at the same time
 - waveform on wire is superposition of forward and reverse traveling wave
 - subtract transmitted wave at each end to recover received wave
- There are 3-levels on the line but its still 2-level signaling
- Much more sensitive to reflections and crosstalk (as if only one end of the line were terminated)

Simultaneous Bidirectional Signaling

The Circuit

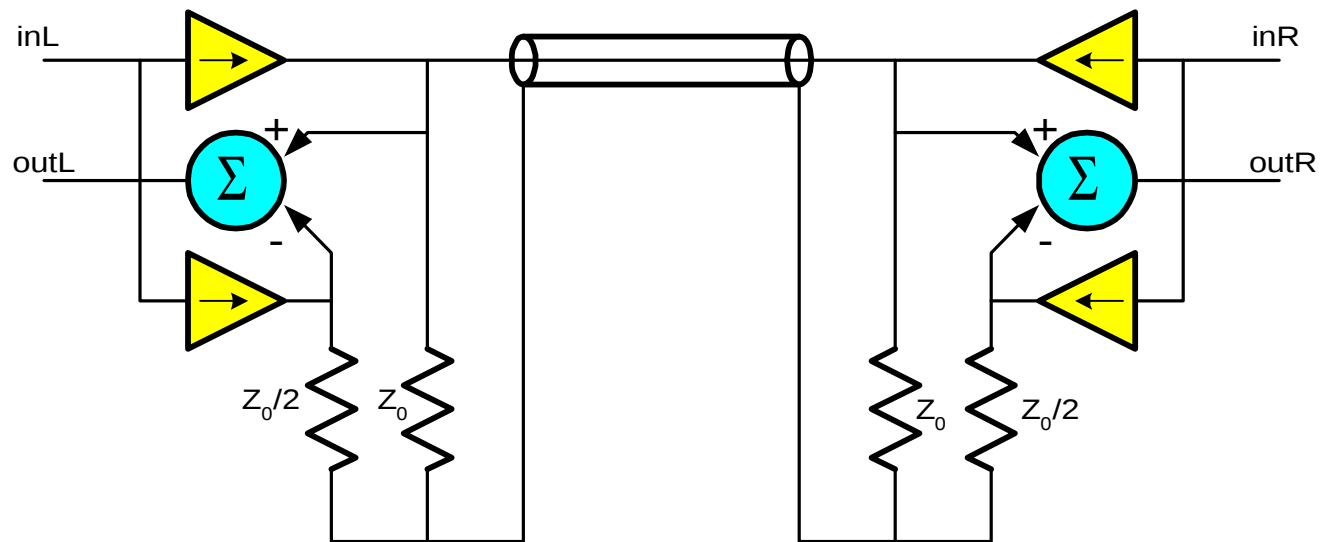

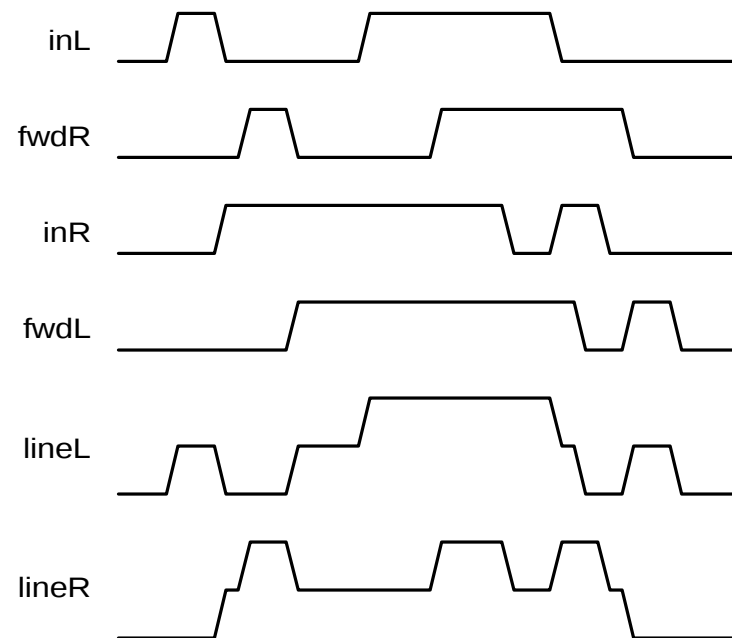Simultaneous Bidirectional Signaling Waveforms



Next Time

- Timing